

# Lecture 6


## Arithmetic for Computers (1)

CS202 2023 Spring

# Today's Agenda


- Recap
- Context
  - Operations on integers
    - Addition and subtraction
    - ALU
    - Dealing with overflow
    - Multiplication and division
- Reading: Textbook 3.1-3.4

# Recap

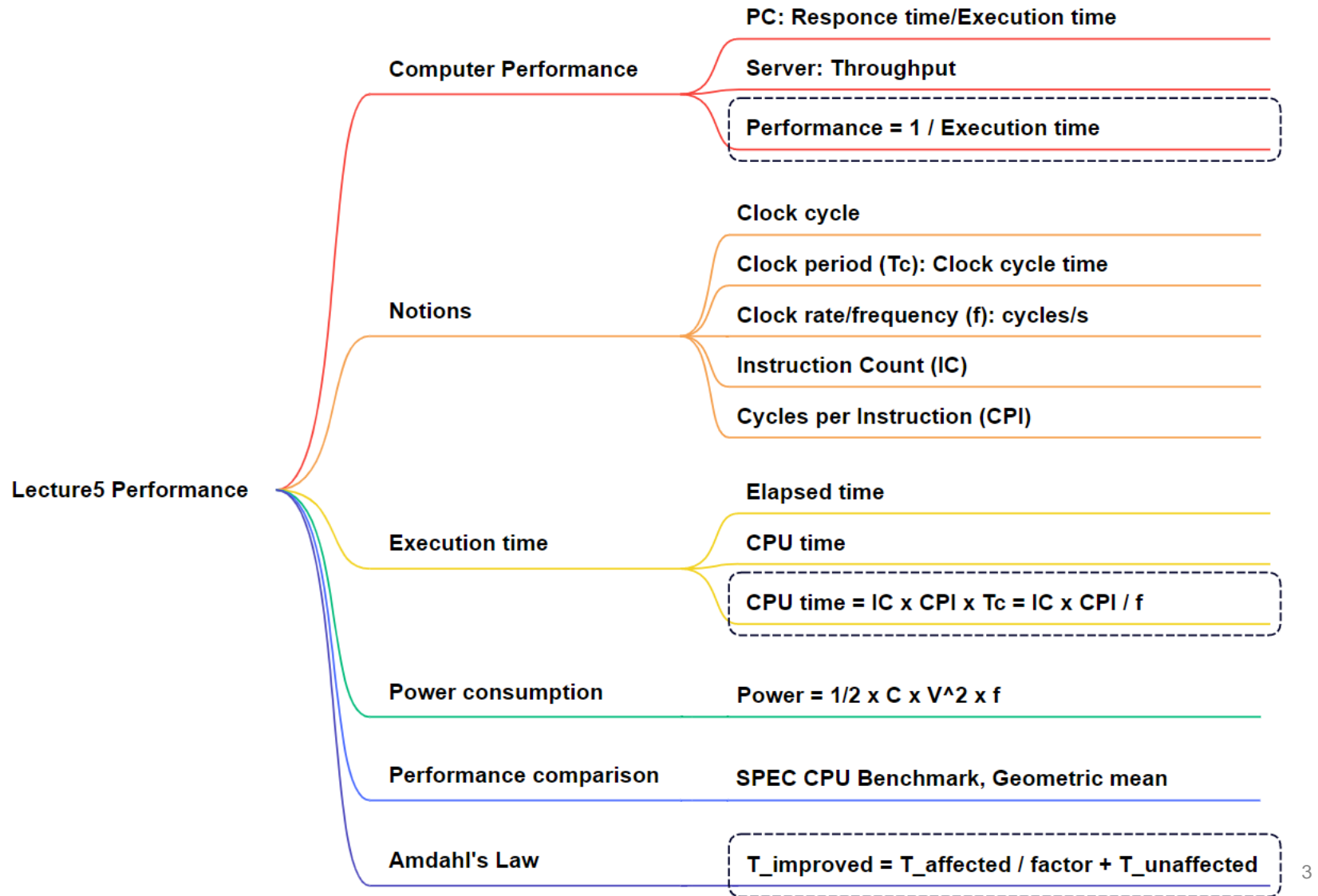

 
# Basic Arithmetic Logic Unit


- One-bit ALU that performs AND, OR, and addition



1-bit logical unit for AND and OR

 


1-bit adder

 

$op = 0, o = a \& b$  (AND)  
 $op = 1, o = a \mid b$  (OR)  
 $op = 2, o = a + b$  (ADD)
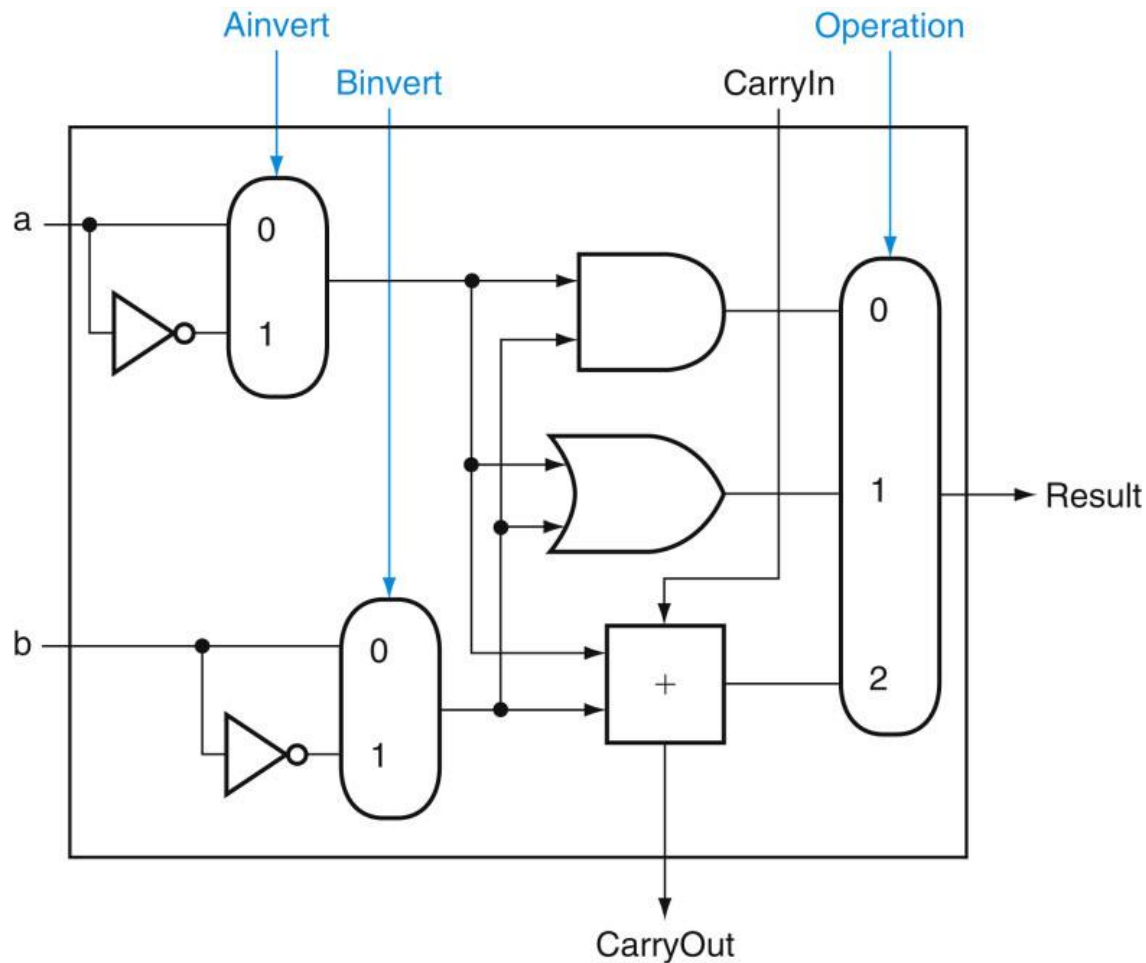
# Enhanced Arithmetic Logic Unit


- ALU that have NAND/NOR operation, and subtraction



1-bit ALU that performs AND, OR, and addition on *a* and *b* or *a'* and *b'*


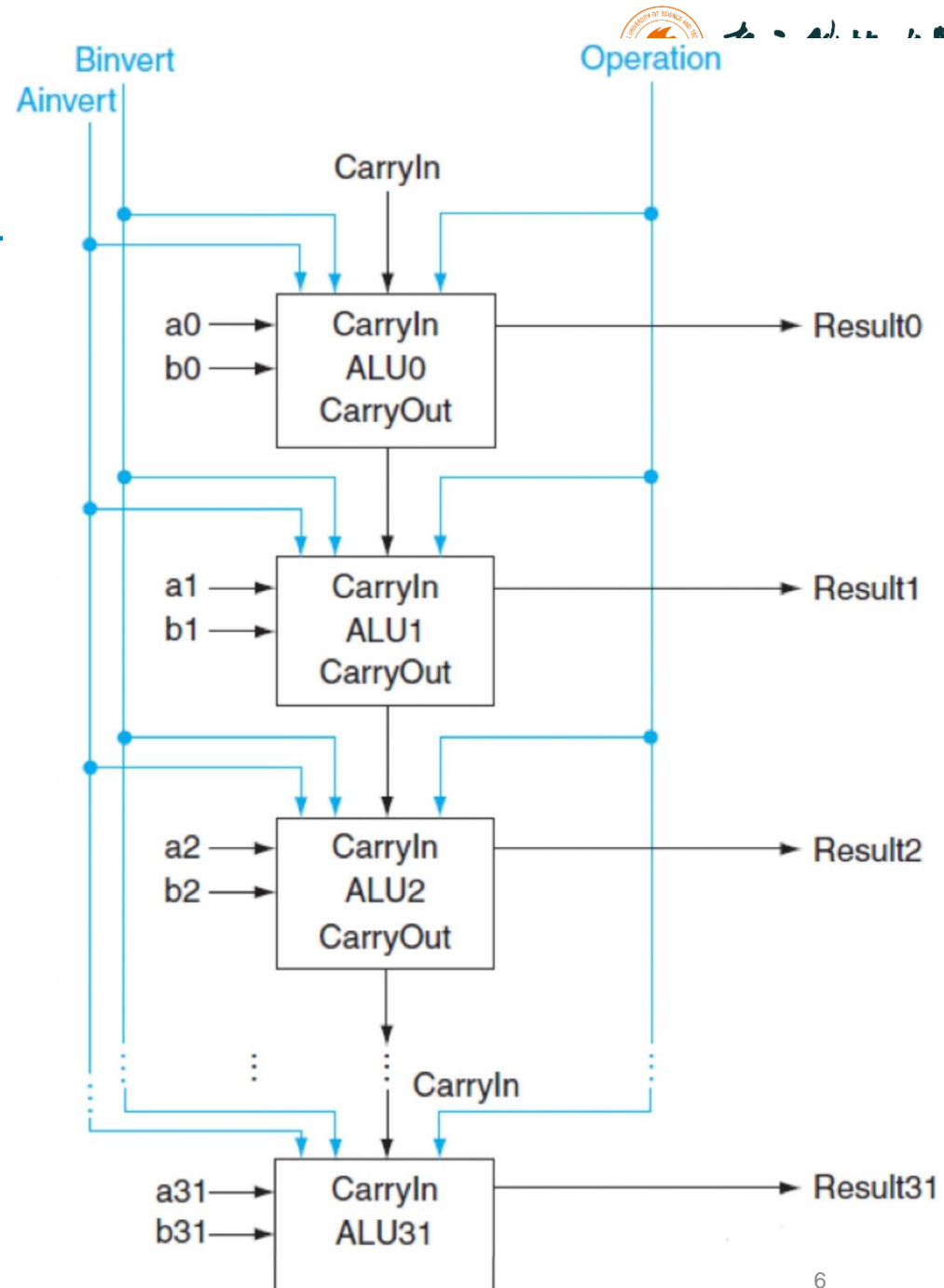
# 32-bit ALU

- Ripple-Carry-Adder
- CarryOut of the less significant bit is connected to the CarryIn of the more significant bit.



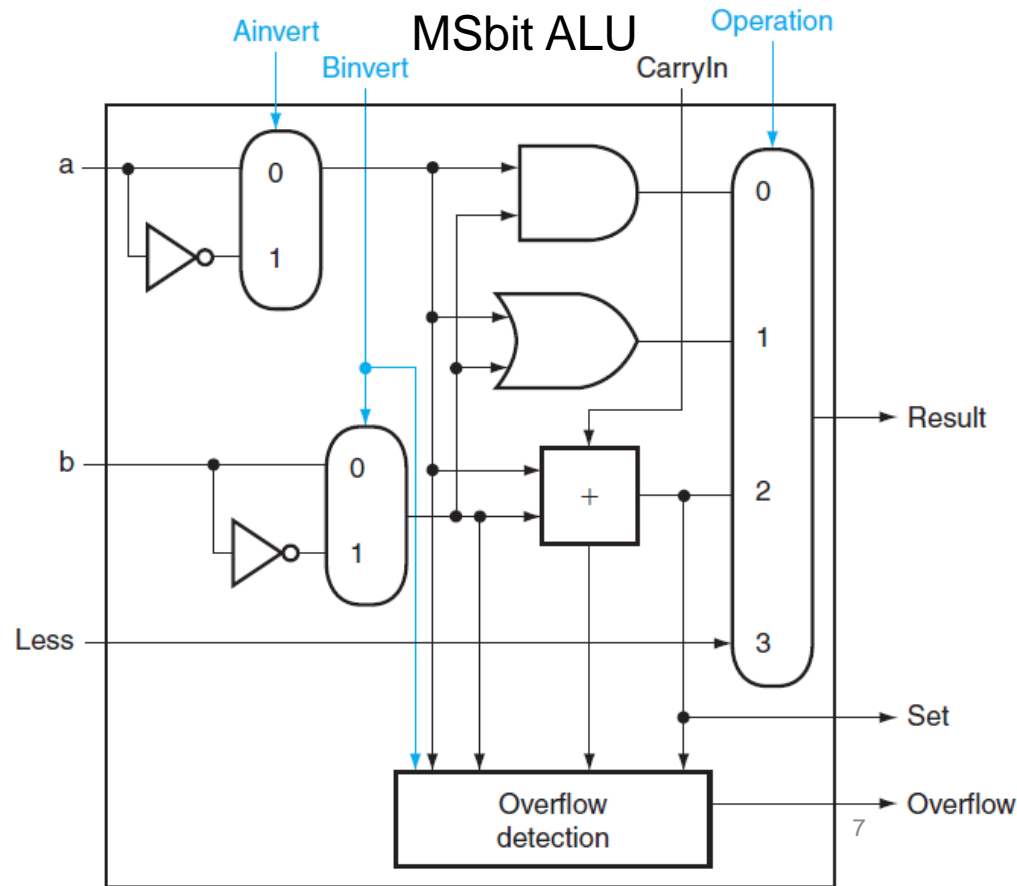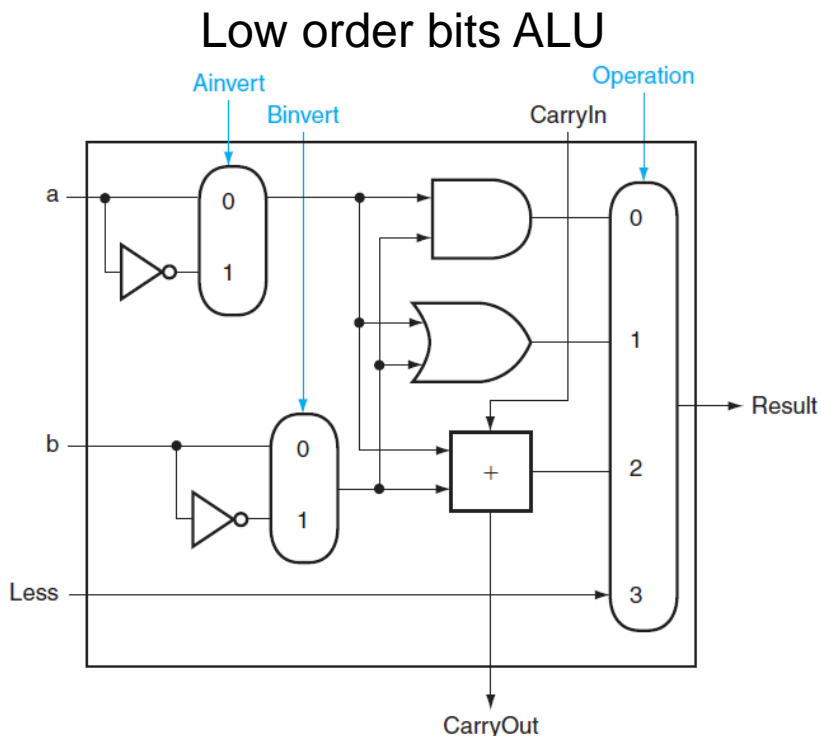
# One-bit ALUs with Set Less Than

- Slt instruction requires a subtraction and then sets all but the LSbit to 0, with the LSbit set to 1 if  $a < b$
- Less signal line
  - Isb – signed bit
  - 1 if  $a < b$ , 0 otherwise


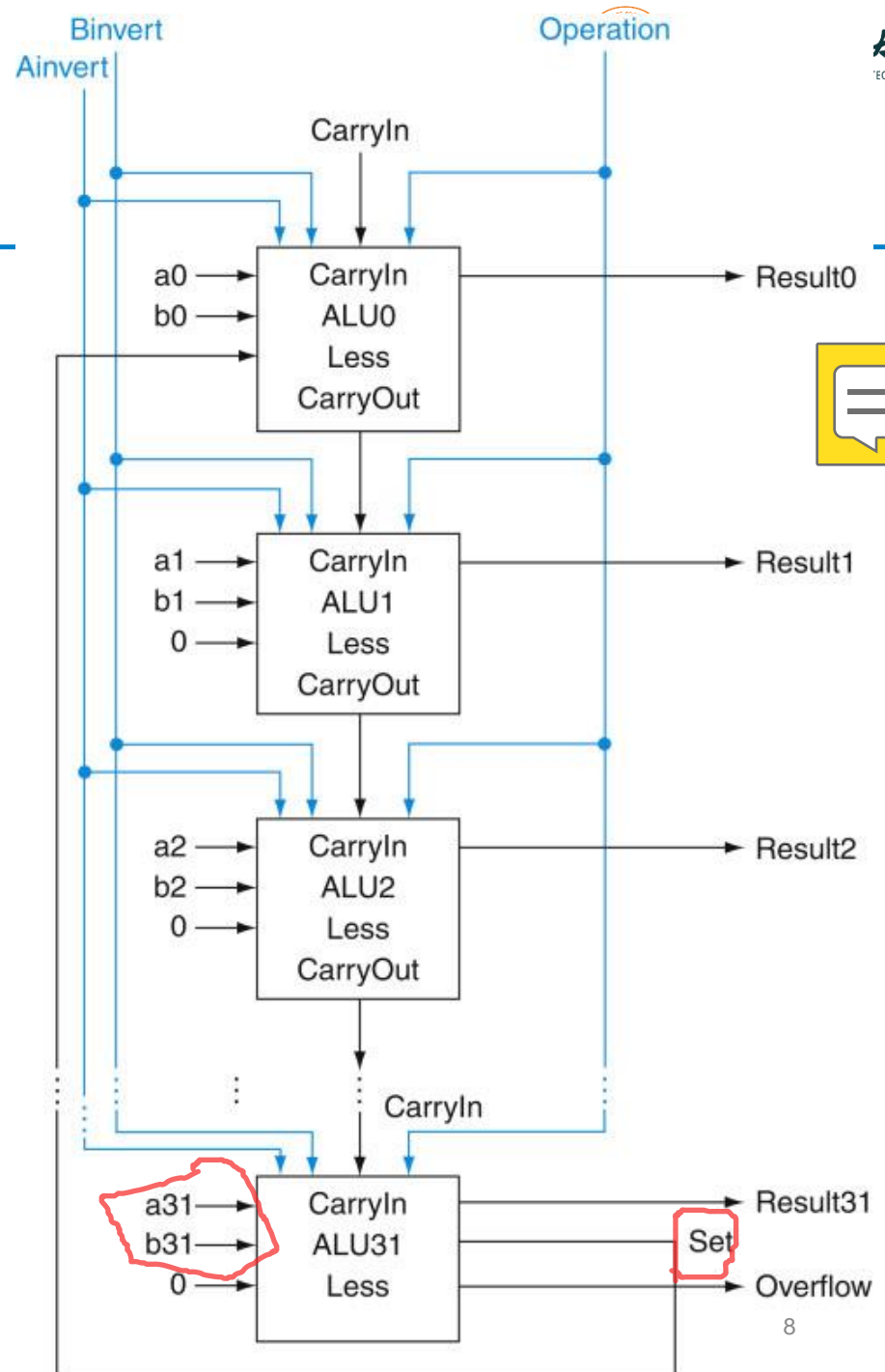
# 32-bit ALU with Set Less Than



- The Less inputs are connected to 0 except for the least significant bit, which is connected to the Set output of the most significant bit.
- If the ALU performs  $a - b$  and we select the input 3 in the multiplexor
  - Result = 0 ... 001 if  $a < b$
  - Result = 0 ... 000 otherwise






# Final 32-bit ALU

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR

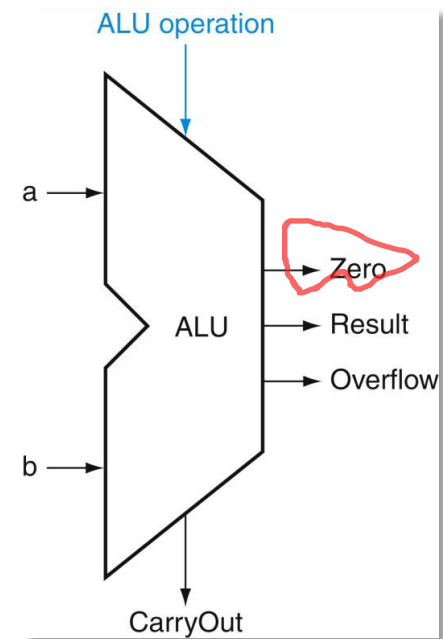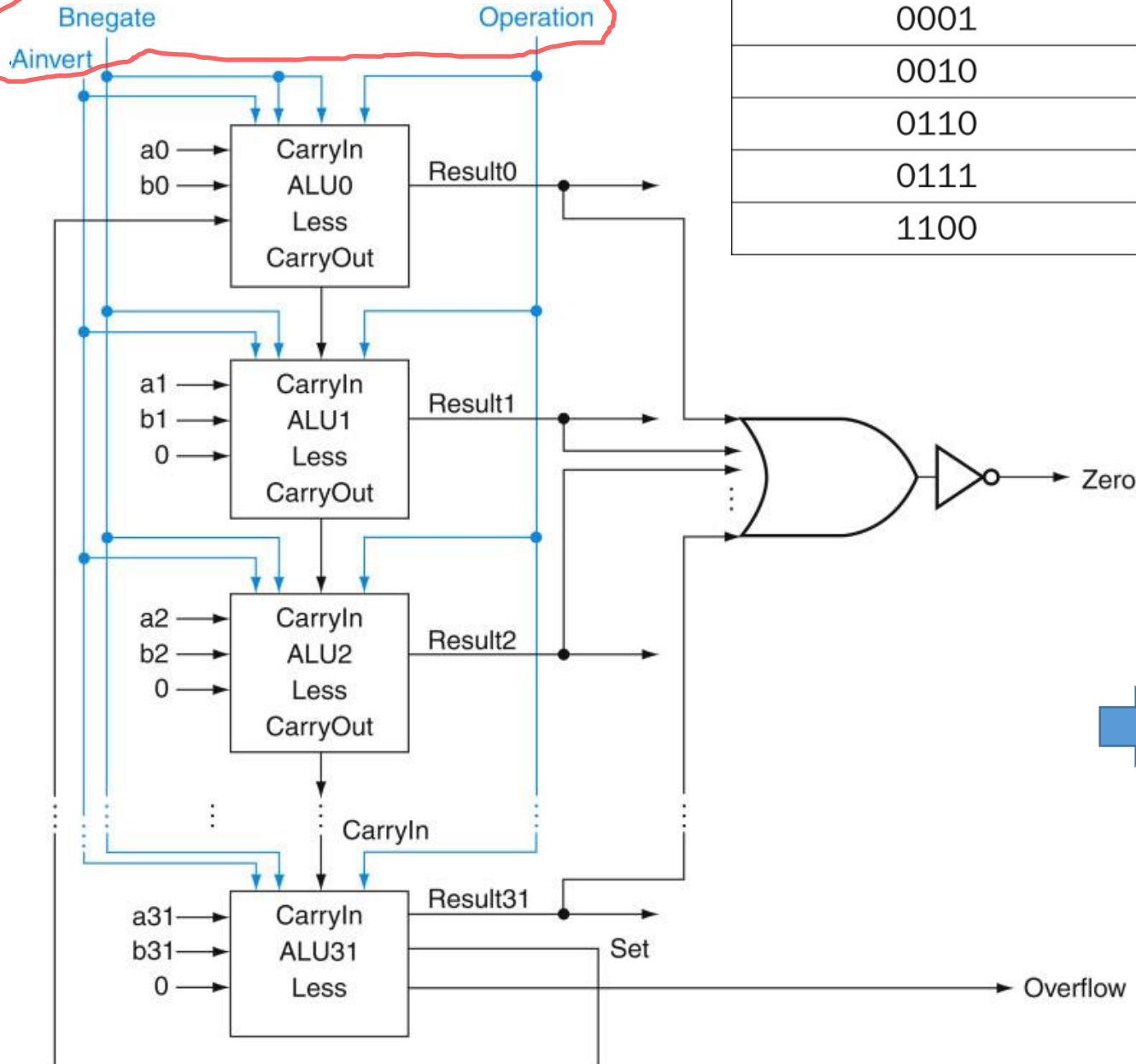

# Integer Addition

## • Example: 7 + 6

 

## • Overflow if result out of range

- Adding +ve and -ve operands, no overflow
- Adding two +ve operands
  - Overflow if result sign is 1
- Adding two -ve operands
  - Overflow if result sign is 0

溢出：1. 正数加正数是负数，比如111+111 结果是1000  
2. 负数+负数是正数

# Integer Subtraction

- Add negation of second operand

- Example:  $7 - 6 = 7 + (-6)$

+7:	0000 0000 ... 0000 0111
-6:	1111 1111 ... 1111 1010
<hr/>	
+1:	0000 0000 ... 0000 0001

- Overflow if result out of range
  - Subtracting two +ve or two -ve operands, no overflow
  - Subtracting +ve from -ve operand
    - Overflow if result sign is 1
  - Subtracting -ve from +ve operand
    - Overflow if result sign is 0

# Integer Addition/Subtraction with Overflow

## • Example:

- $12+3=15$  (00001100+00000011)
- $120+15=135$  (01111000+00001111)
- $12-3=9$  (00001100-00000011)
- $-100-50=-150$  (10011100-00110010)

$$\begin{array}{r} 00001100 \\ + 00000011 \\ \hline 00001111 \end{array}$$

$$\begin{array}{r} 01111000 \\ + 00001111 \\ \hline 10000111 \end{array}$$

$$\begin{array}{r} 00001100 \\ + 11111101 \\ \hline 00001001 \end{array}$$

$$\begin{array}{r} 10011100 \\ + 11001110 \\ \hline 01101010 \end{array}$$

Overflow

# Dealing with Overflow

- Some languages (e.g., C) ignore overflow
  - Use MIPS `addu`, `addiu`, `subu` instructions
- Other languages (e.g., Ada, Fortran) require raising an exception
  - Use MIPS `add`, `addi`, `sub` instructions
  - On overflow, invoke exception handler
    - Save PC in exception program counter (EPC) register
    - Jump to predefined handler address
    - `mfc0` (move from coprocessor reg) instruction can retrieve EPC value, to return after corrective action
- Note: `addiu`: “u” means it doesn't generate overflow exception, but the immediate can be a signed number

异常处理：先把pc寄存器里面的指令存到EPC里面，跳转到预定义的处理程序地址  
`mfc0`（从协处理器reg移动）指令可以检索EPC值，并在纠正操作后返回

# Overflow Detection for Signed & Unsigned Addition

- Signed addition

```
addu $t0, $t1, $t2      # $t0 = sum
xor $t3, $t1, $t2      # Check if signs differ
slt $t3, $t3, $zero     # $t3 = 1 if signs differ
bne $t3, $zero, No_overflow # $t1, $t2 signs ≠, no overflow
xor $t3, $t0, $t1      # $t1, $t2 signs =, check sum
slt $t3, $t3, $zero     # $t3 = 1 if sum sign ≠
bne $t3, $zero, Overflow # All 3 signs ≠; goto overflow
```

- Unsigned addition

```
addu $t0, $t1, $t2      # $t0 = sum
nor $t3, $t1, $zero     # $t3 = NOT $t1
sltu $t3, $t3, $t2      #  $(2^{32} - \$t1 - 1) < \$t2$ 
bne $t3, $zero, Overflow # if  $(2^{32}-1 < \$t1+\$t2)$ , overflow
```

同号才会可能溢出，先判断是否同号，按位异或，如果符号位不同结果为1，为1的话t3就是负数，去和0比较，如果是负数，说明t1，t2同号，然后t0去和t1比较，如果同号说明没有溢出

# Arithmetic for Multimedia

- Graphics and media processing operates on vectors of 8-bit and 16-bit data
  - Use 64-bit adder, with partitioned carry chain
    - Operate on  $8 \times 8$ -bit,  $4 \times 16$ -bit, or  $2 \times 32$ -bit vectors
  - SIMD (single-instruction, multiple-data)
- Saturating operations
  - On overflow, result is largest representable value
    - c.f. 2s-complement modulo arithmetic
  - E.g., clipping in audio, saturation in video

# Multiplication

- In every step
  - multiplicand is shifted
  - next bit of multiplier is examined (also a shifting step)
  - if this bit is 1, shifted multiplicand is added to the product

mul ti pi cand : 被乘数  
mul ti pl ier : 乘数

multiplicand


multiplier

```

      1000
    × 1001
    -----
      1000
     0000
    0000
   1000
  -----
 1001000
    
```

product

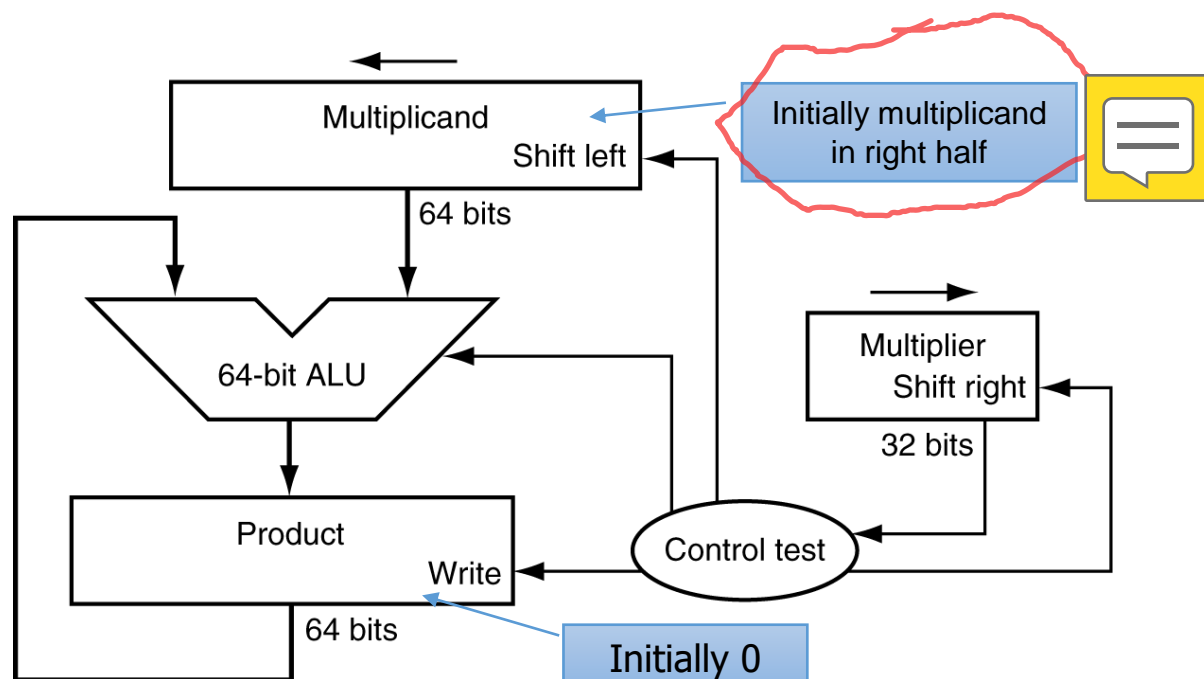
Length of product is  
the sum of operand  
lengths





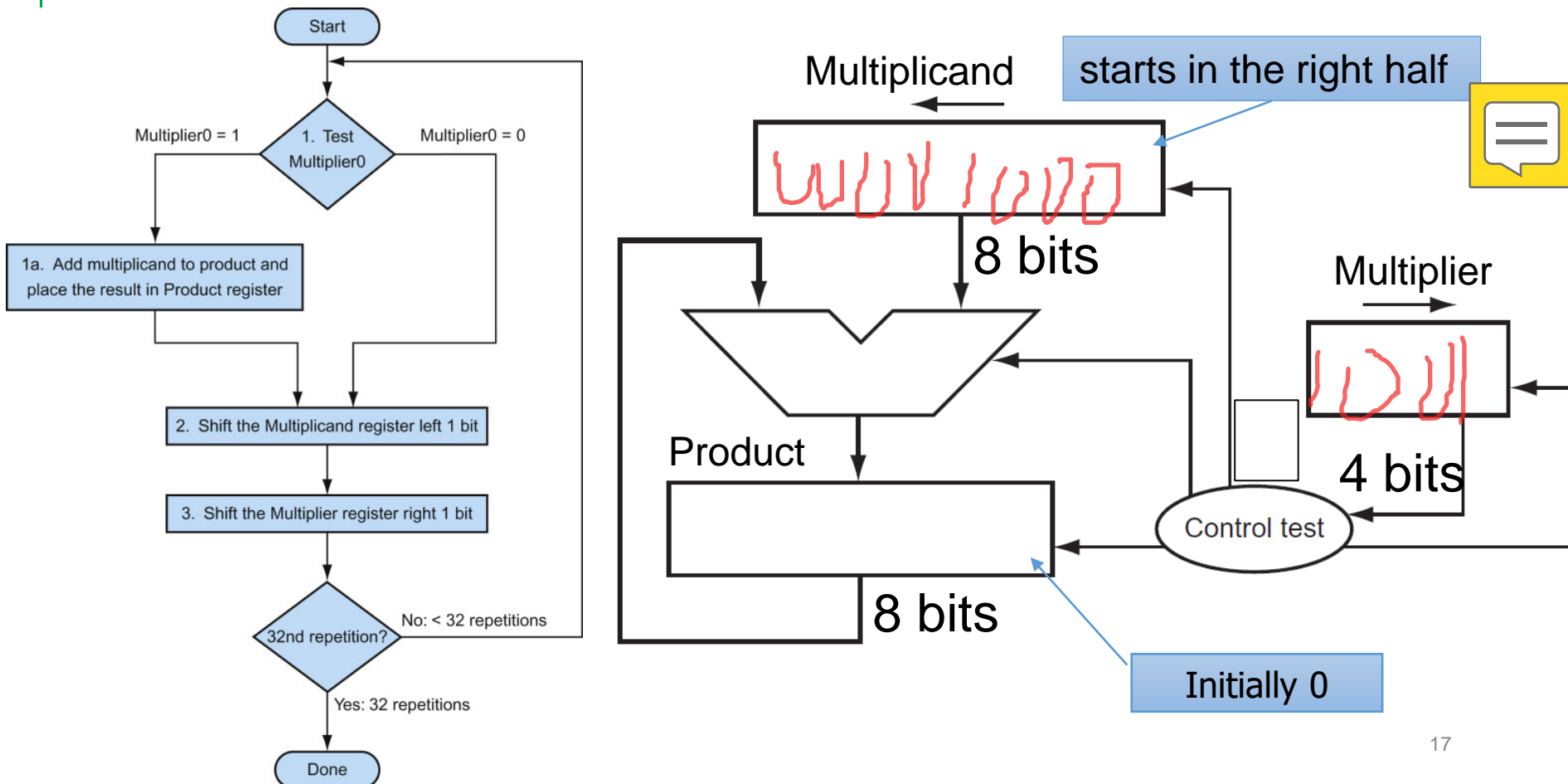
# Multiplication Example

- Multiply  $8_{\text{ten}}$  ( $1000_{\text{two}}$ ) by  $9_{\text{ten}}$  ( $1001_{\text{two}}$ )
  - How values change in Mcand, Mplier and Product Registers?



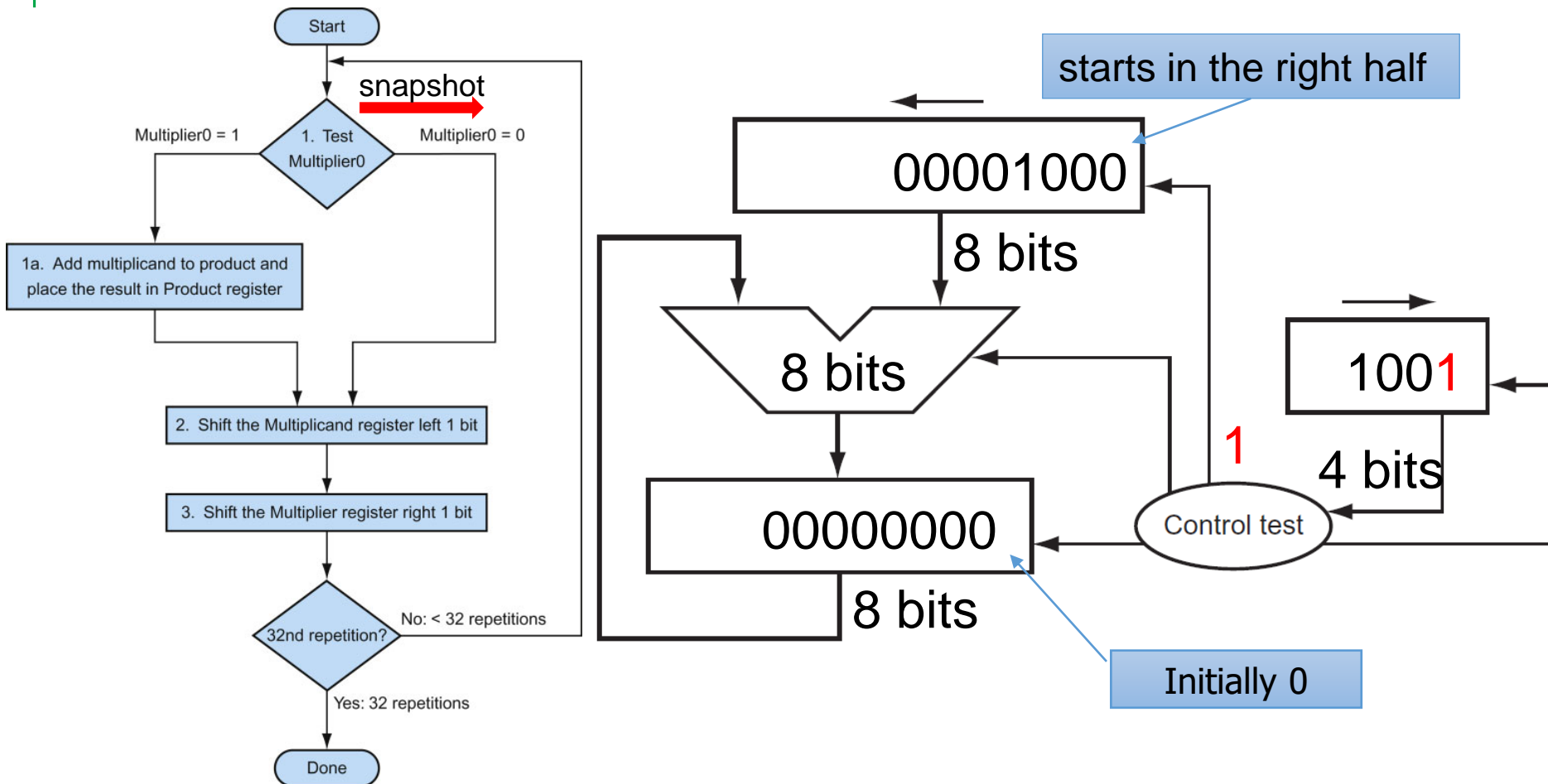
# Multiplication Example

- Multiply  $8_{\text{ten}}$  ( $1000_{\text{two}}$ ) by  $9_{\text{ten}}$  ( $1001_{\text{two}}$ )



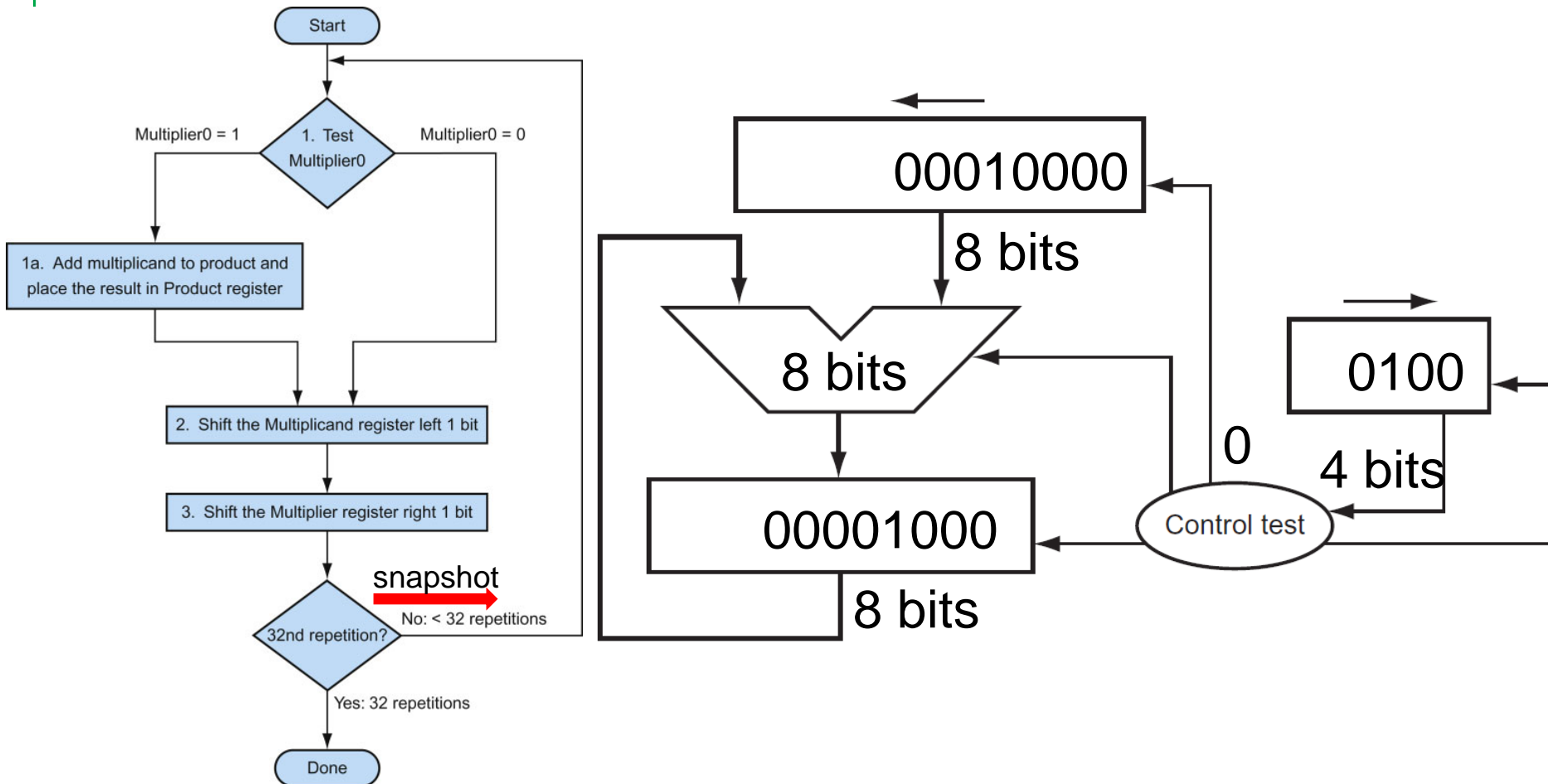
# Multiplication Example

- Multiply  $8_{\text{ten}}$  ( $1000_{\text{two}}$ ) by  $9_{\text{ten}}$  ( $1001_{\text{two}}$ )



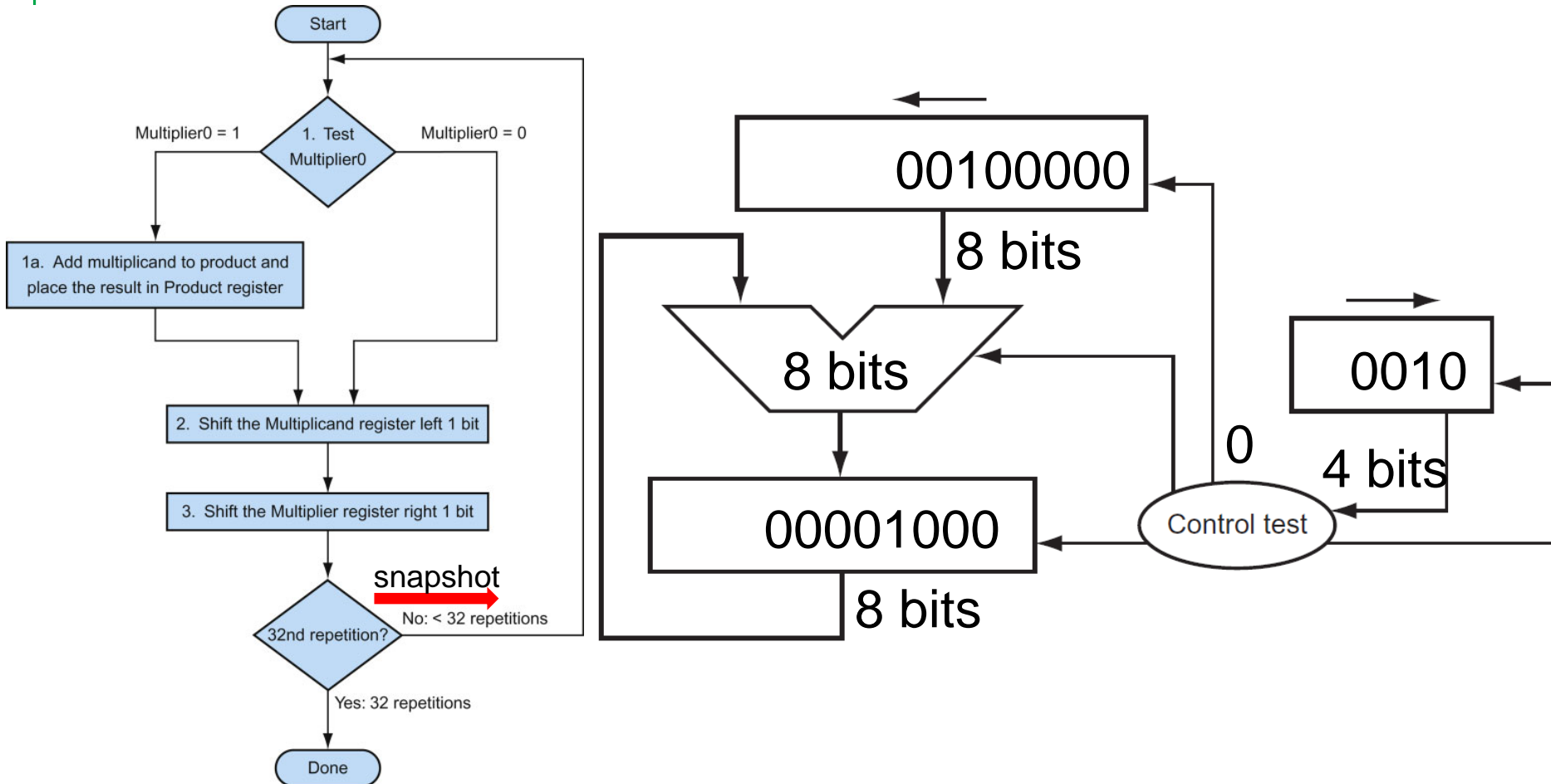
# Multiplication Example

- Multiply  $8_{\text{ten}}$  ( $1000_{\text{two}}$ ) by  $9_{\text{ten}}$  ( $1001_{\text{two}}$ )



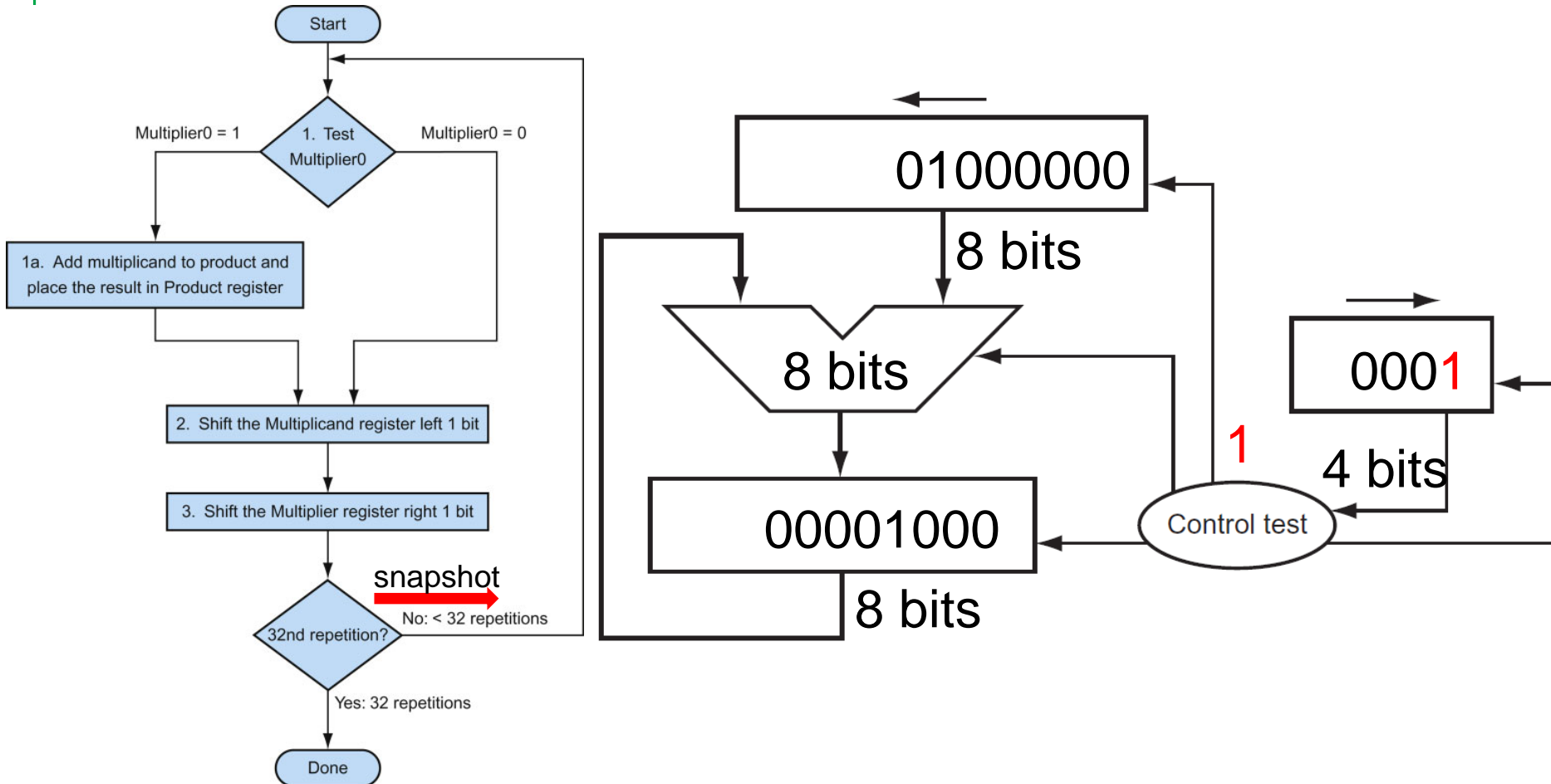
# Multiplication Example

- Multiply  $8_{\text{ten}}$  ( $1000_{\text{two}}$ ) by  $9_{\text{ten}}$  ( $1001_{\text{two}}$ )


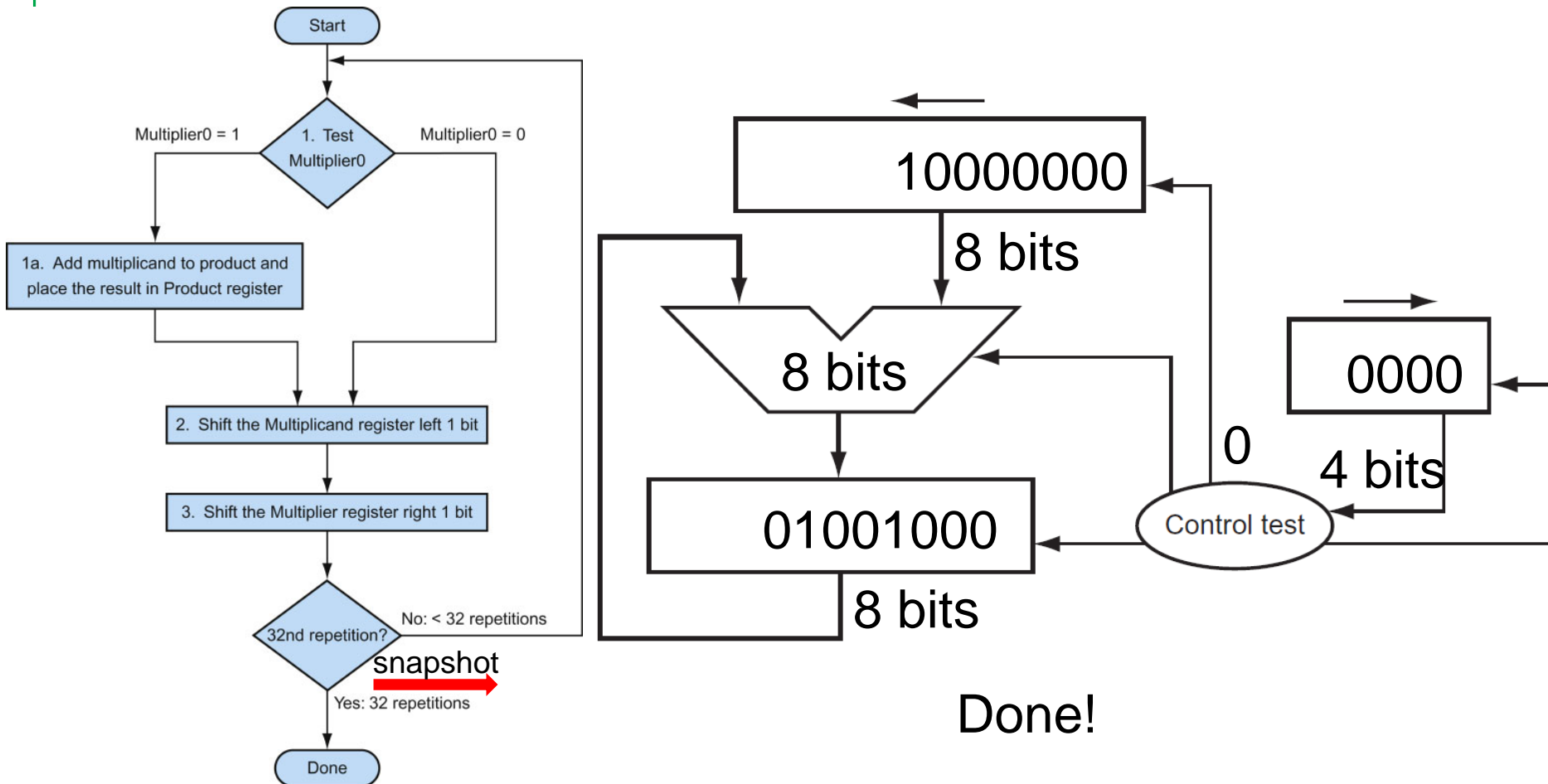
# Multiplication Example

- Multiply  $8_{\text{ten}}$  ( $1000_{\text{two}}$ ) by  $9_{\text{ten}}$  ( $1001_{\text{two}}$ )





# Multiplication Example

- Multiply  $8_{\text{ten}}$  ( $1000_{\text{two}}$ ) by  $9_{\text{ten}}$  ( $1001_{\text{two}}$ )

Iter	Step	Multiplier	Multiplicand	Product
0	Initial values	100 <b>1</b>	0000 1000	0000 0000
1	1 $\Rightarrow$ Prod = Prod + Mcand Shift left Multiplicand Shift right Multiplier	1001 1001 <b>0100</b>	0000 1000 <b>0001 0000</b> 0001 0000	<b>0000 1000</b> 0000 1000 0000 1000
2	0 $\Rightarrow$ No operation Shift left Multiplicand Shift right Multiplier	0100 0100 <b>0010</b>	0001 0000 <b>0010 0000</b> 0010 0000	0000 1000 0000 1000 0000 1000
3	Same steps as 2	0010 0010 <b>0001</b>	0010 0000 <b>0100 0000</b> 0100 0000	0000 1000 0000 1000 0000 1000
4	Same steps as 1	0001 0001 <b>0000</b>	0100 0000 <b>1000 0000</b> 1000 0000	<b>0100 1000</b> 0100 1000 0100 1000
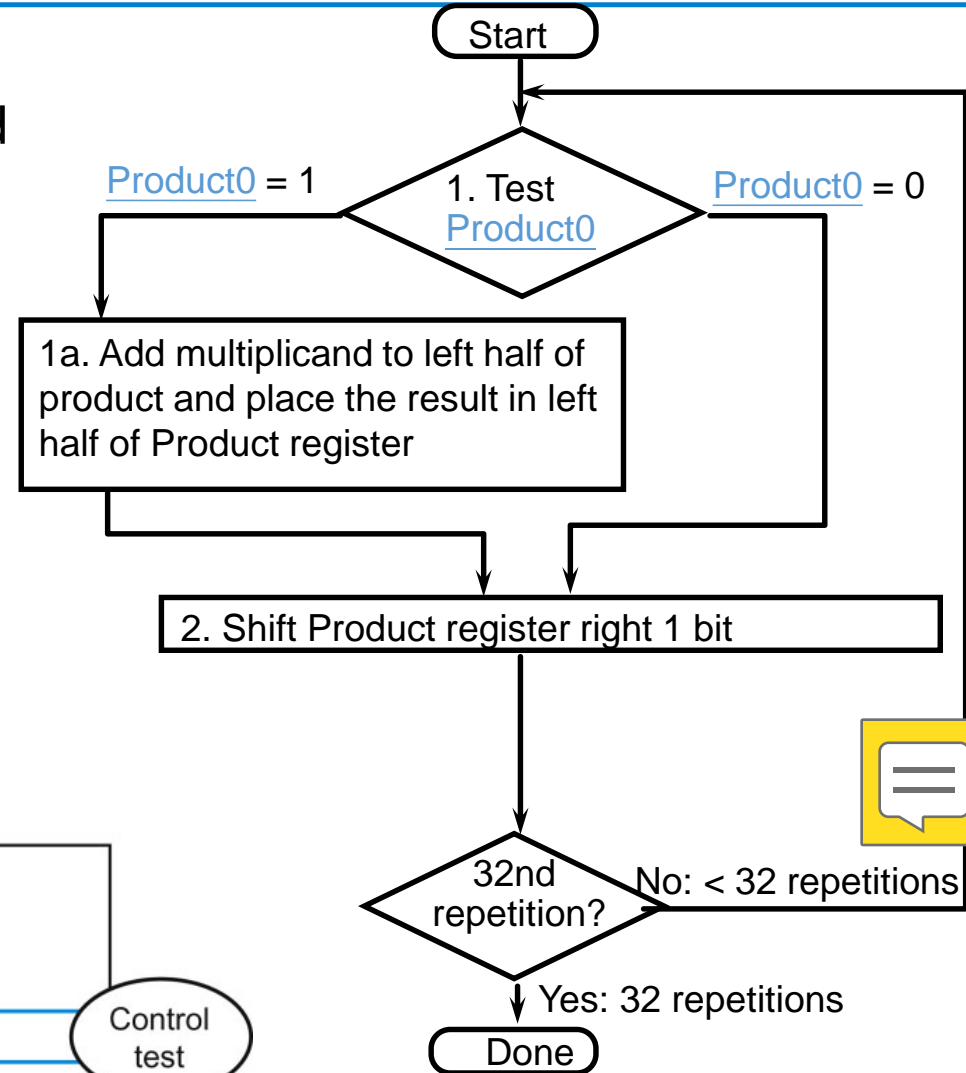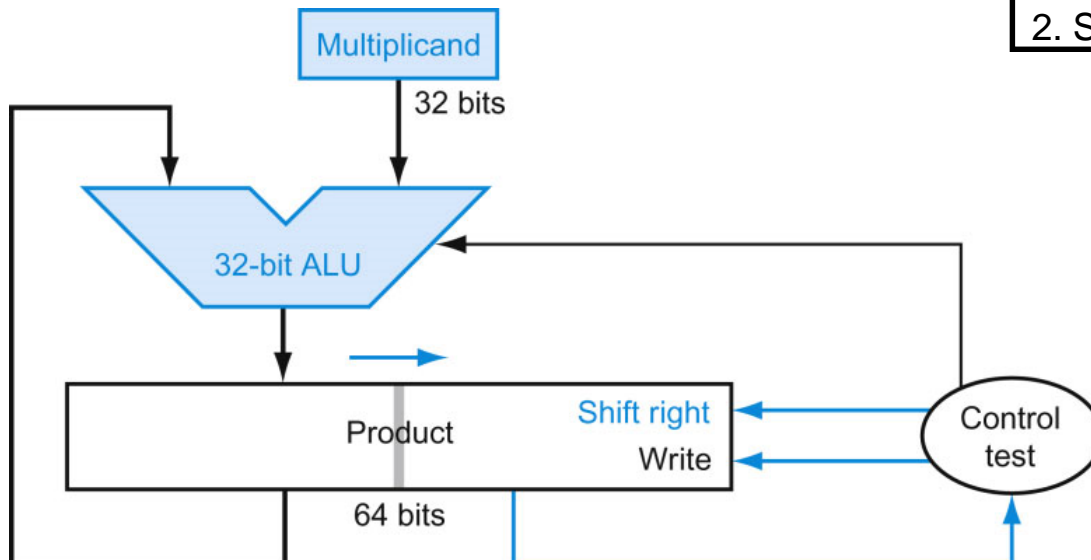
# Optimized Multiplier Hardware


- Multiplier initially in right half of product register, 32-bit ALU and multiplicand is untouched
- Check the 0th bit in Product register, if 1, add left half of product with multiplicand
- The sum keeps shifting right, at every step, number of bits in product + multiplier = 64





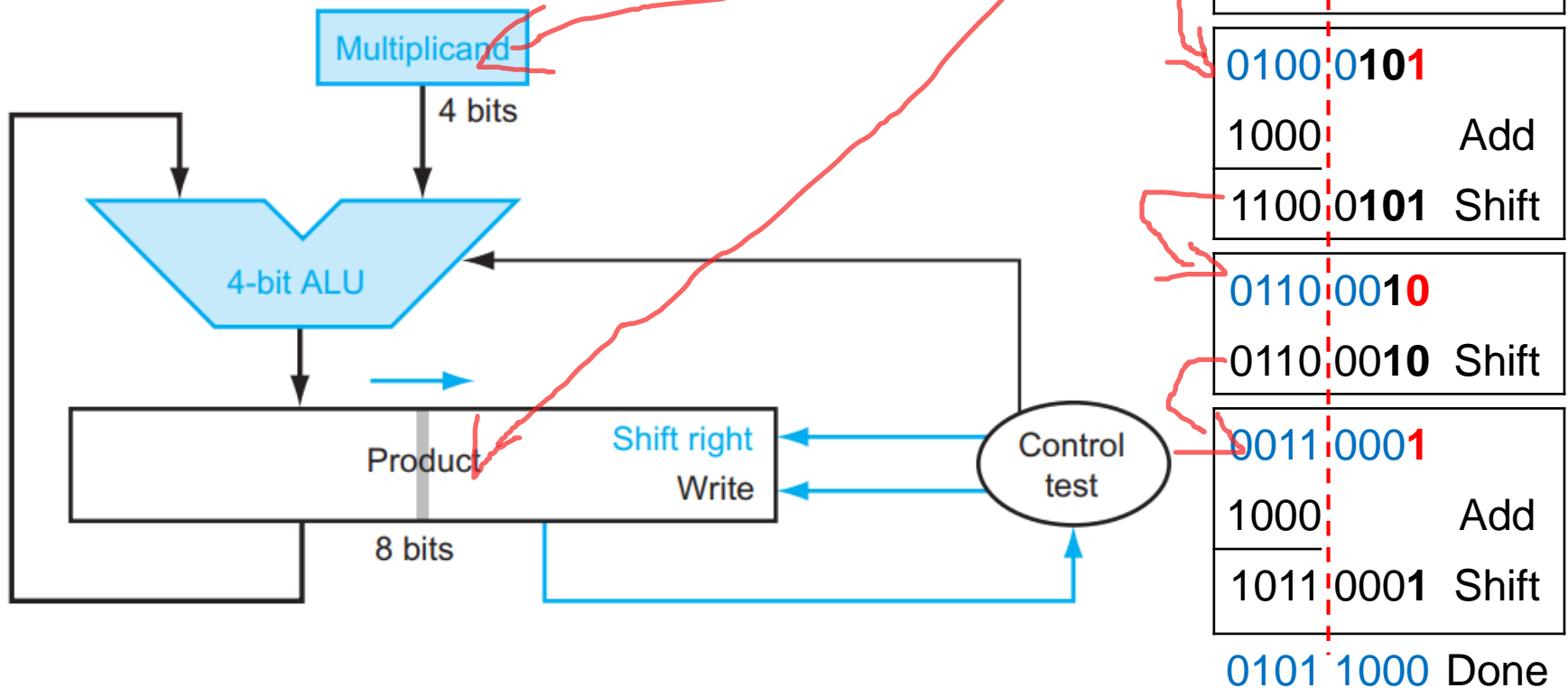
# Optimized Multiplier Example

- Multiply  $8_{\text{ten}}$  ( $1000_{\text{two}}$ ) by  $11_{\text{ten}}$  ( $1011_{\text{two}}$ ) :
- Values in Product register?
- How about Multiplicand register?



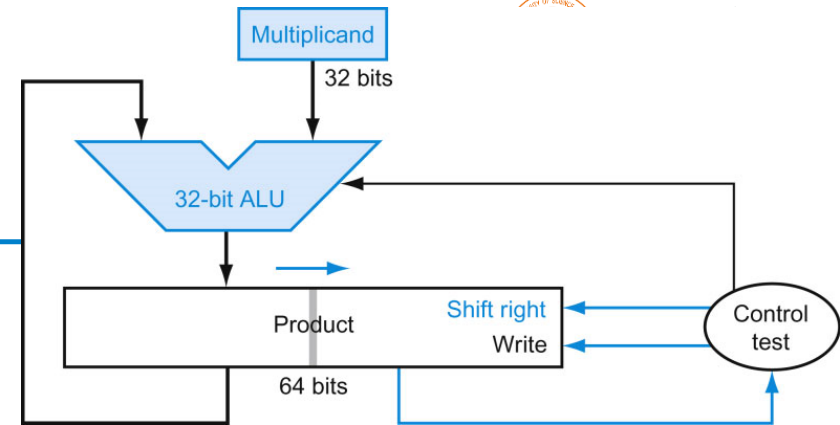- Multiply  $8_{\text{ten}}$  by  $9_{\text{ten}}$  :
- Value in Product Register?
- How about Multiplicand?



4

4




■ ■ ■



---

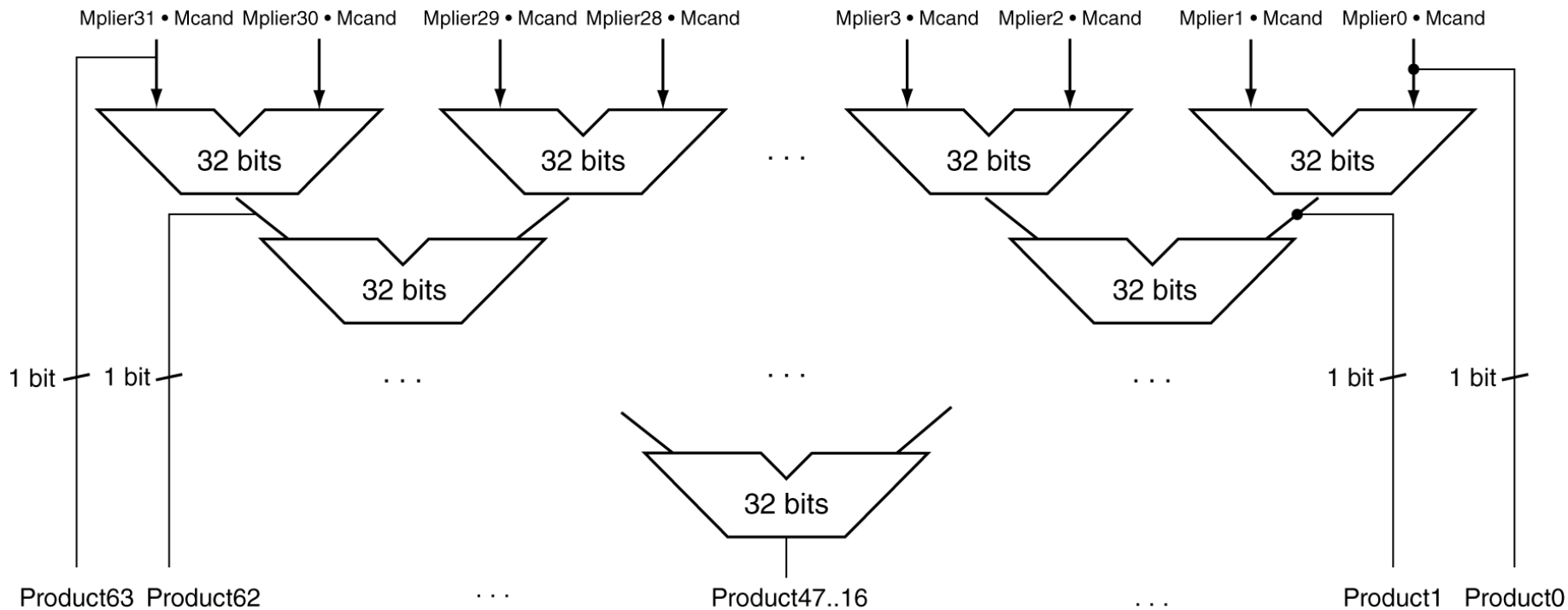
# Faster Multiplier

- Uses multiple adders
  - Cost/performance tradeoff
  - Can be pipelined
  - Several multiplication performed in parallel



# Faster Multiplier

- 4-bits example

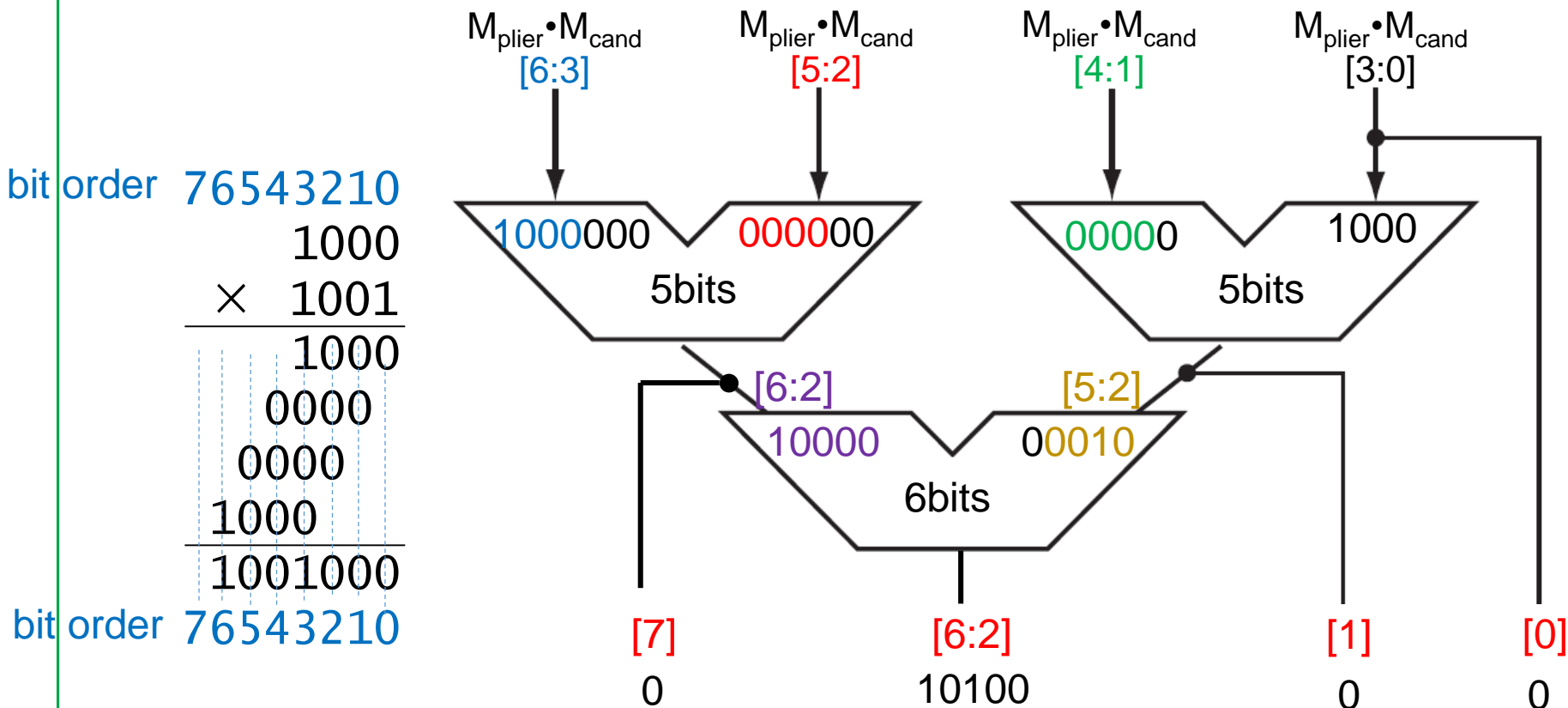

final result: 01001000

# Notes


- The previous algorithm also works for signed numbers (negative numbers in 2's complement form)
- We can also convert negative numbers to positive, multiply the magnitudes, and convert to negative if signs disagree
- The product of two 32-bit numbers can be a 64-bit number
  - hence, in MIPS, the product is saved in two 32-bit registers

# MIPS Multiplication


- Two 32-bit registers for product
  - HI: most-significant 32 bits
  - LO: least-significant 32-bits
- Instructions
  - `mult rs, rt` / `multu rs, rt`
    - 64-bit product in HI/LO
  - `mfhi rd` / `mflo rd`
    - Move from HI/LO to rd
    - Can test HI value to see if product overflows 32 bits
  - `mul rd, rs, rt`
    - Least-significant 32 bits of product → rd
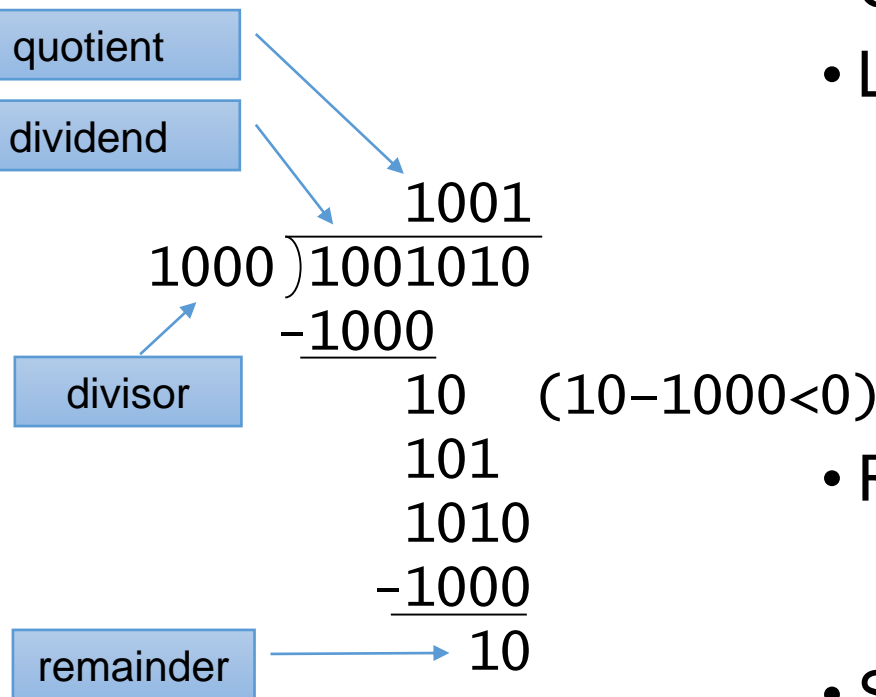
# Division

- Check for 0 divisor
- Long division approach
  - If divisor  $\leq$  dividend bits
    - 1 bit in quotient, subtract
  - Otherwise
    - 0 bit in quotient, bring down next dividend bit
- Restoring division
  - Do the subtract, and if remainder goes  $< 0$ , add divisor back
- Signed division
  - Divide using absolute values
  - Adjust sign of quotient and remainder as required




# Division Hardware

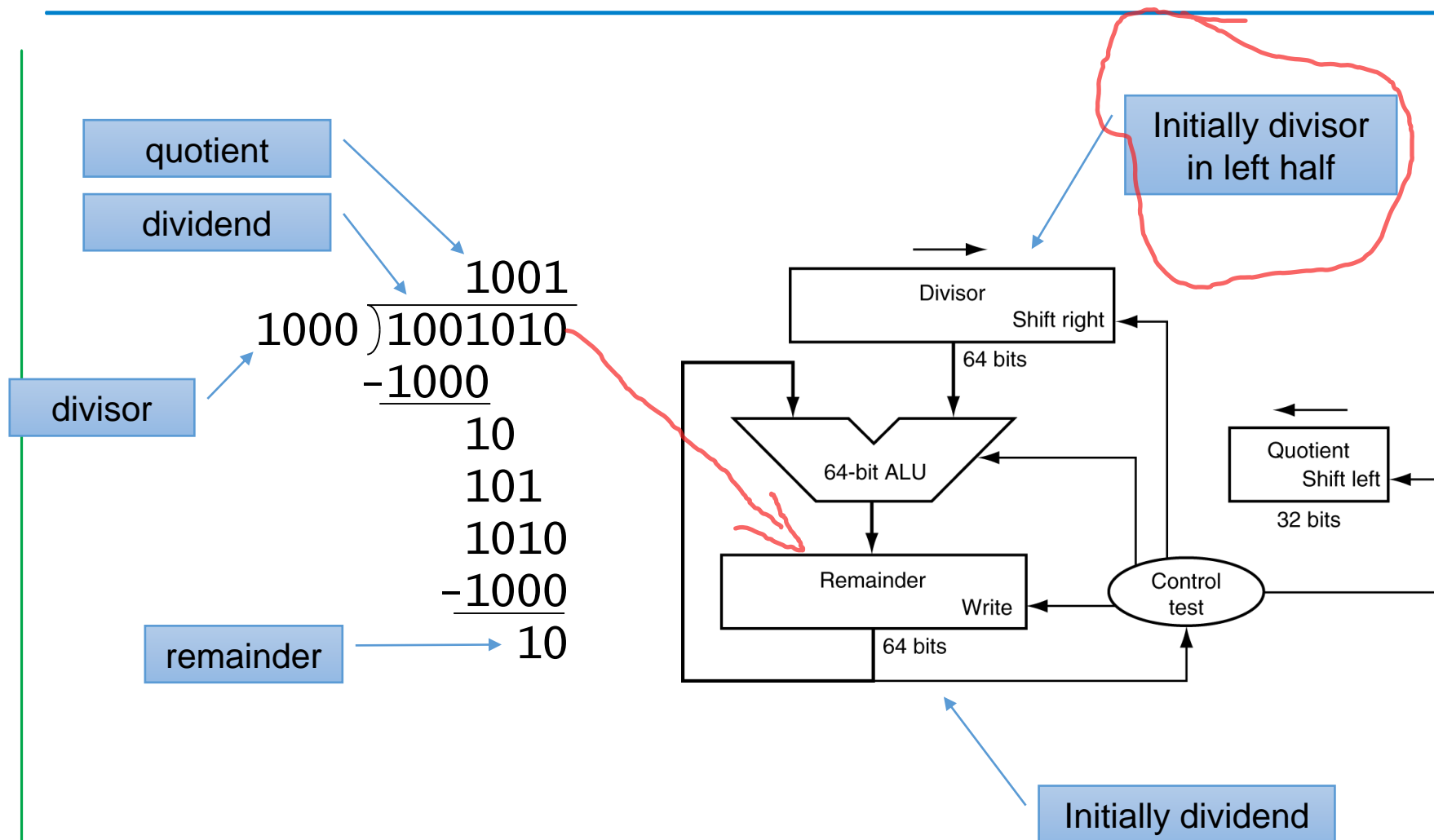



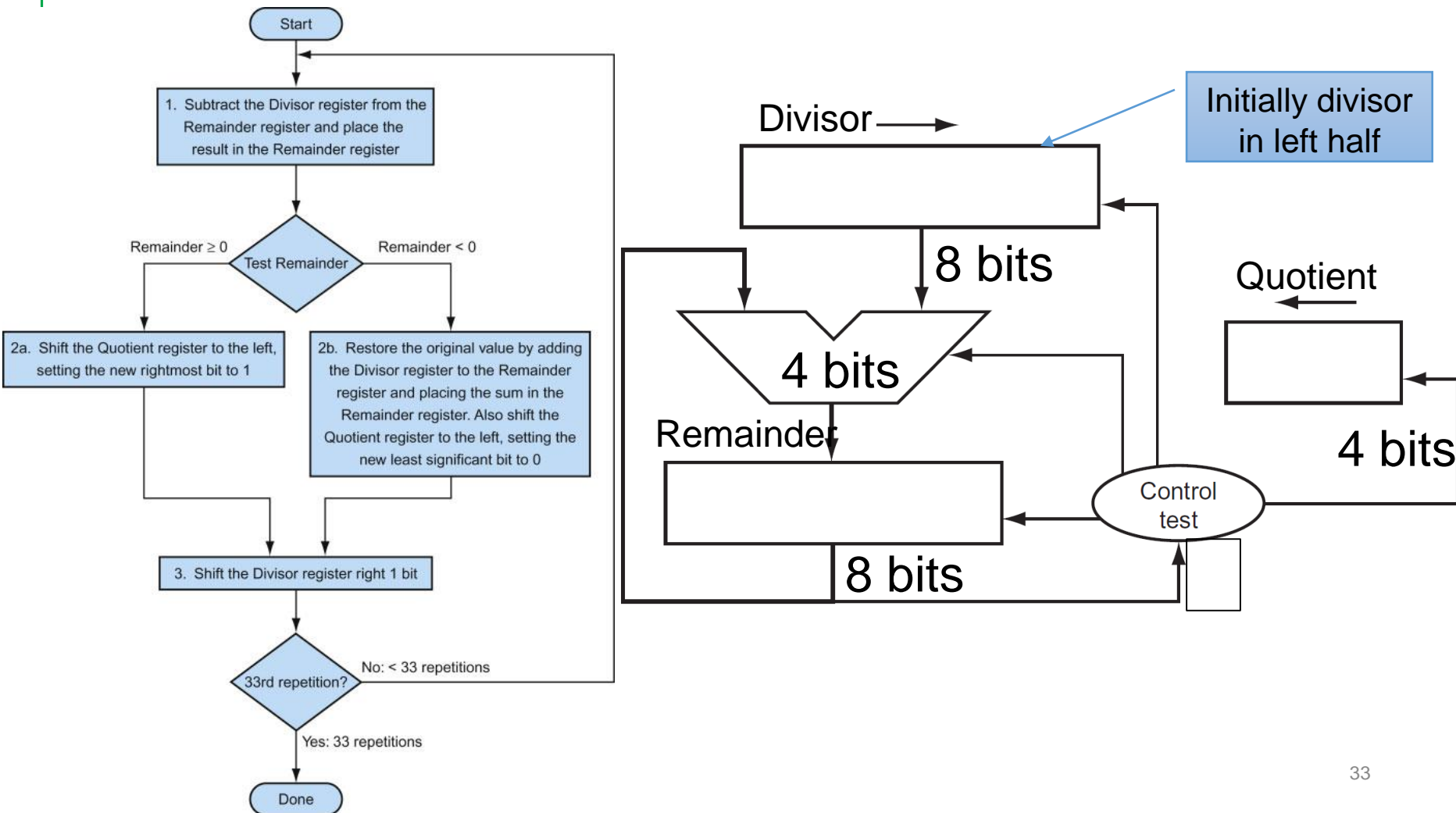
# Division Example

- Divide  $7_{\text{ten}}$  ( $0000\ 0111_{\text{two}}$ ) by  $2_{\text{ten}}$  ( $0010_{\text{two}}$ )




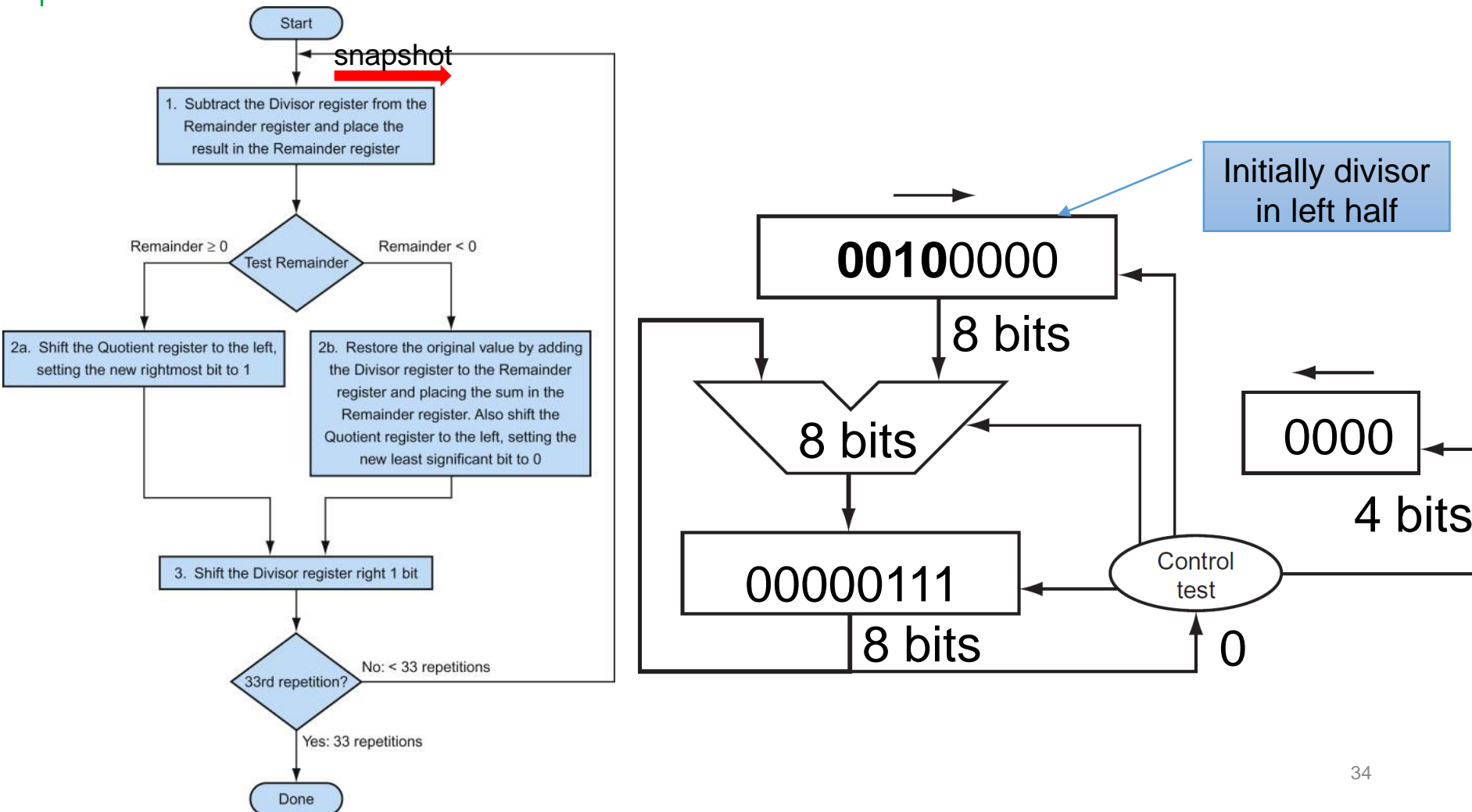
# Division Example

- Divide  $7_{\text{ten}}$  ( $0000\ 0111_{\text{two}}$ ) by  $2_{\text{ten}}$  ( $0010_{\text{two}}$ )



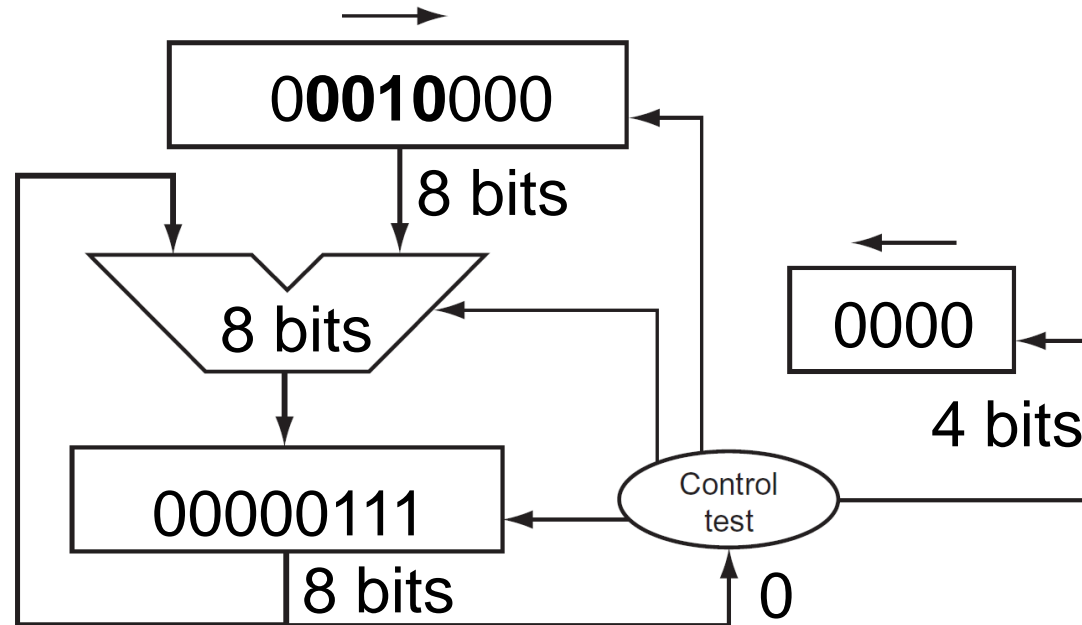
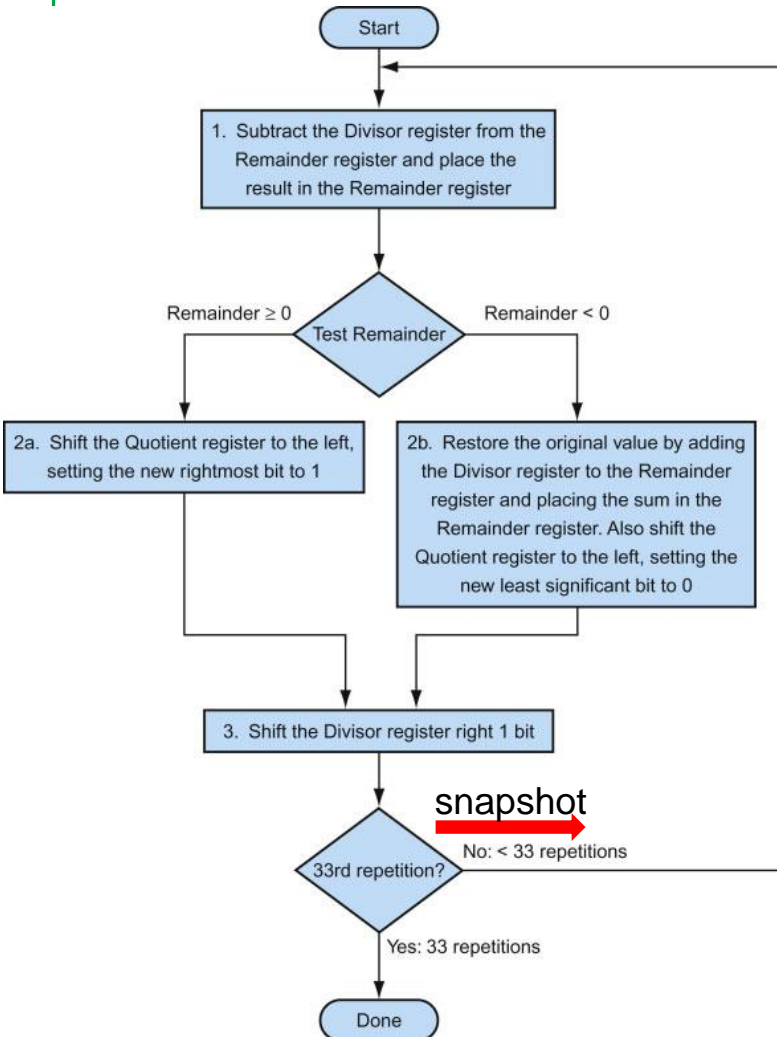
# Division Example

- Divide  $7_{\text{ten}}$  ( $0000\ 0111_{\text{two}}$ ) by  $2_{\text{ten}}$  ( $0010_{\text{two}}$ )



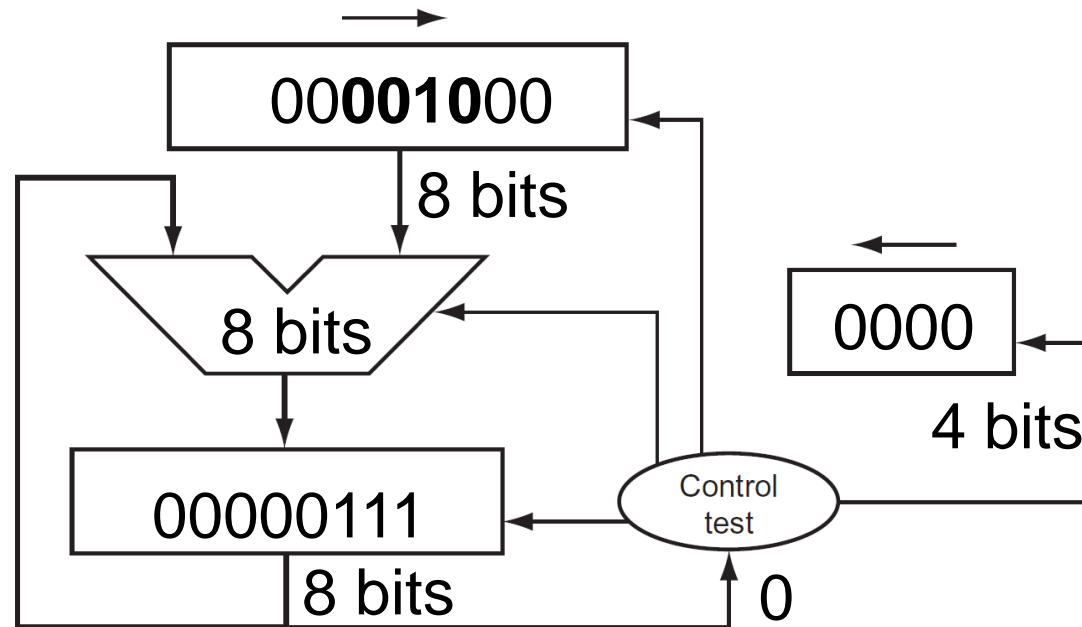
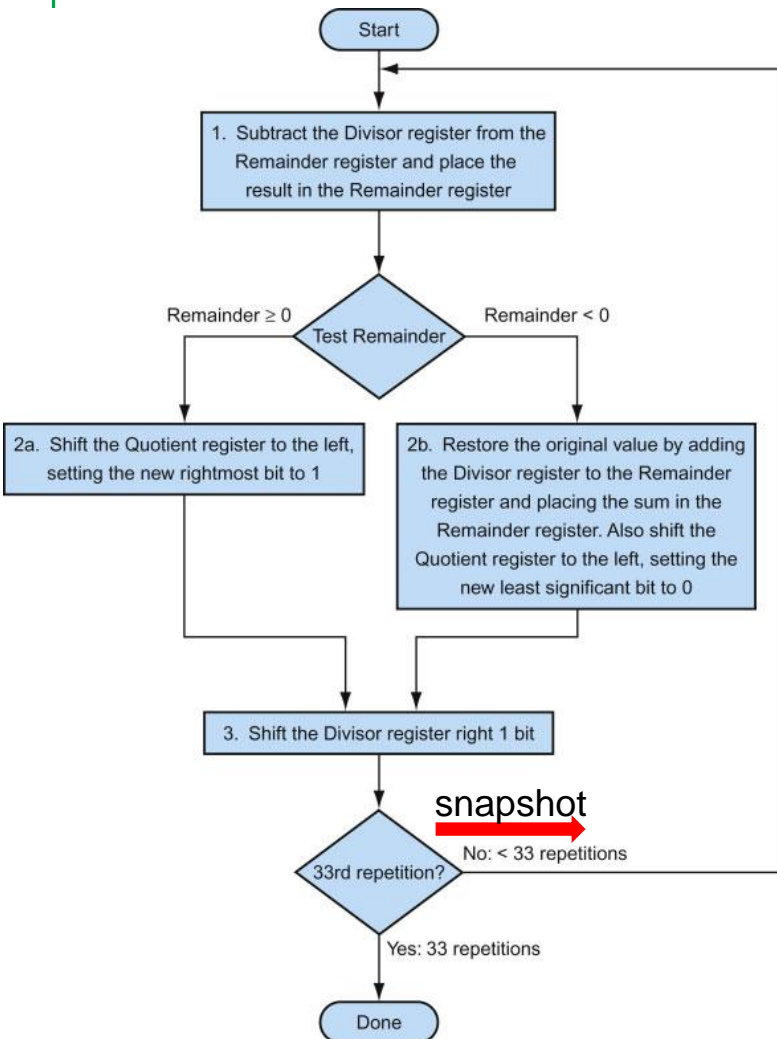
# Division Example

- Divide  $7_{\text{ten}}$  ( $0000\ 0111_{\text{two}}$ ) by  $2_{\text{ten}}$  ( $0010_{\text{two}}$ )



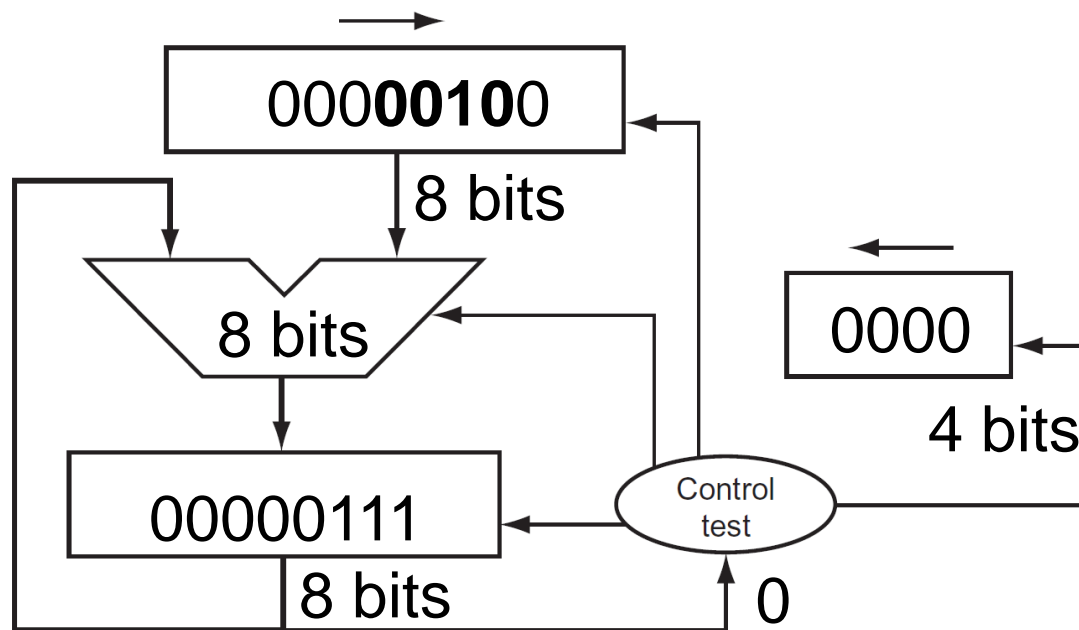
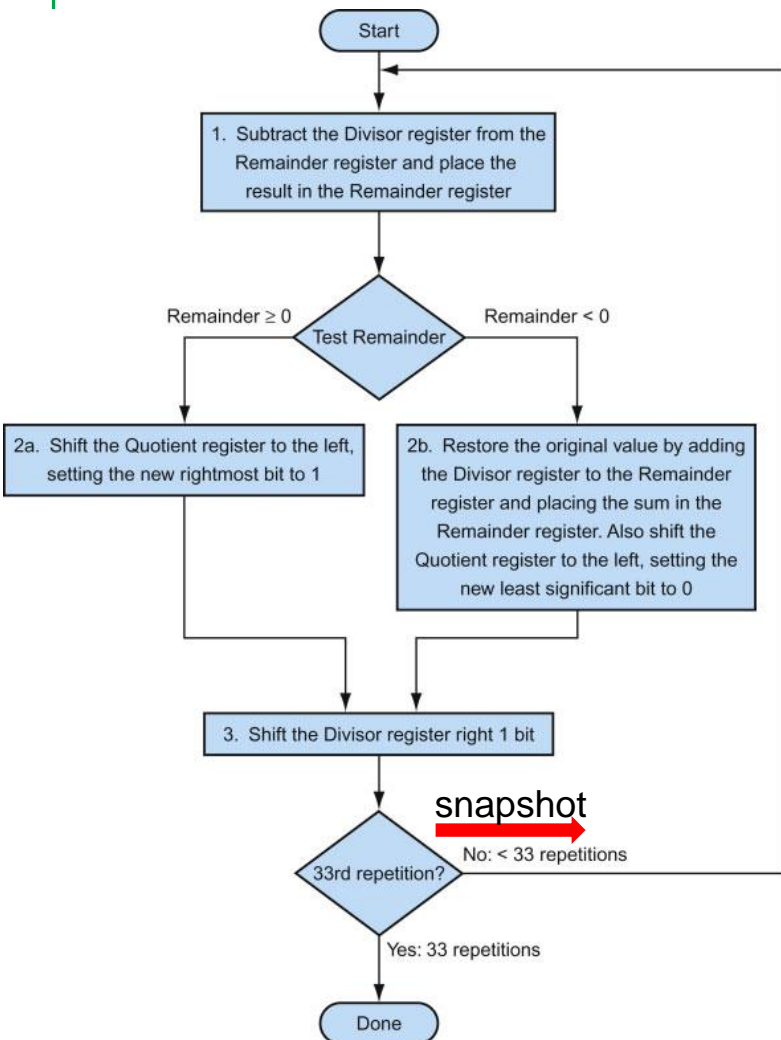
# Division Example

- Divide  $7_{\text{ten}}$  ( $0000\ 0111_{\text{two}}$ ) by  $2_{\text{ten}}$  ( $0010_{\text{two}}$ )



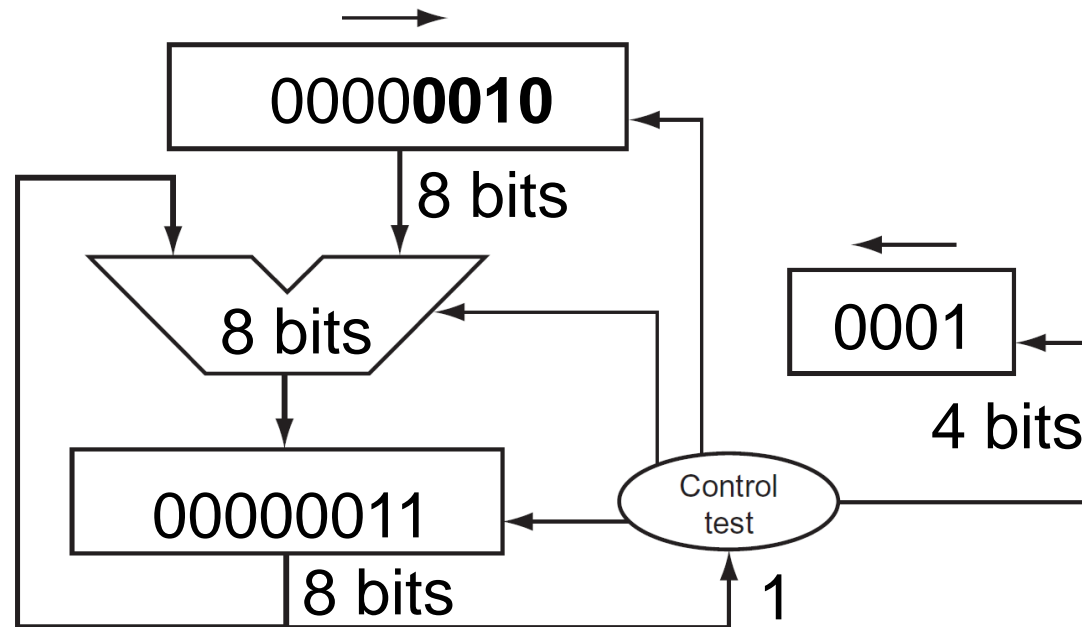
 
# Division Example

- Divide  $7_{\text{ten}}$  ( $0000\ 0111_{\text{two}}$ ) by  $2_{\text{ten}}$  ( $0010_{\text{two}}$ )


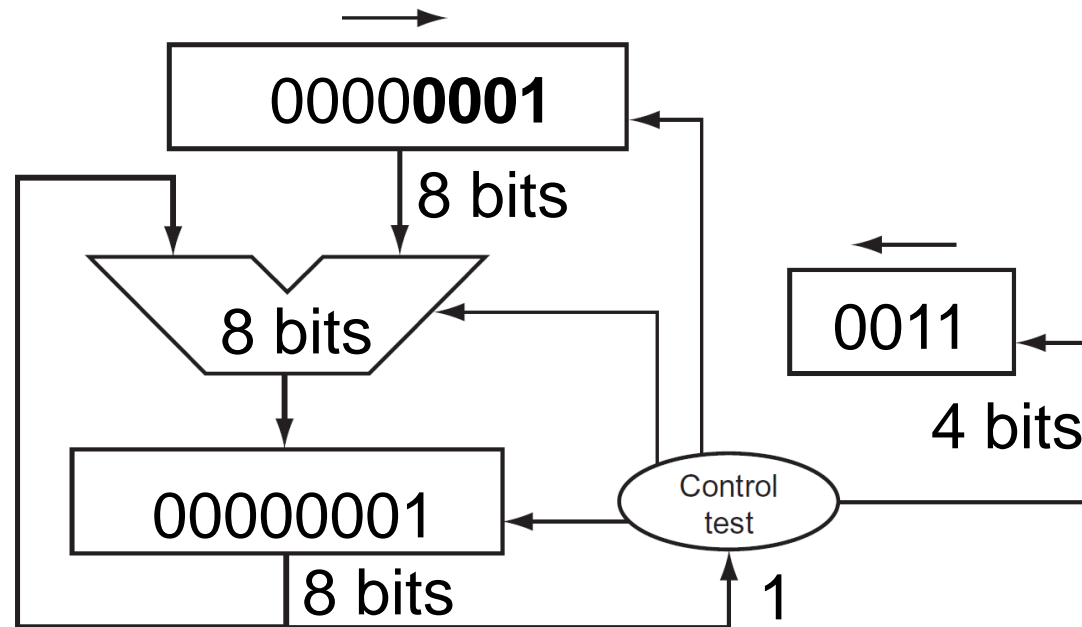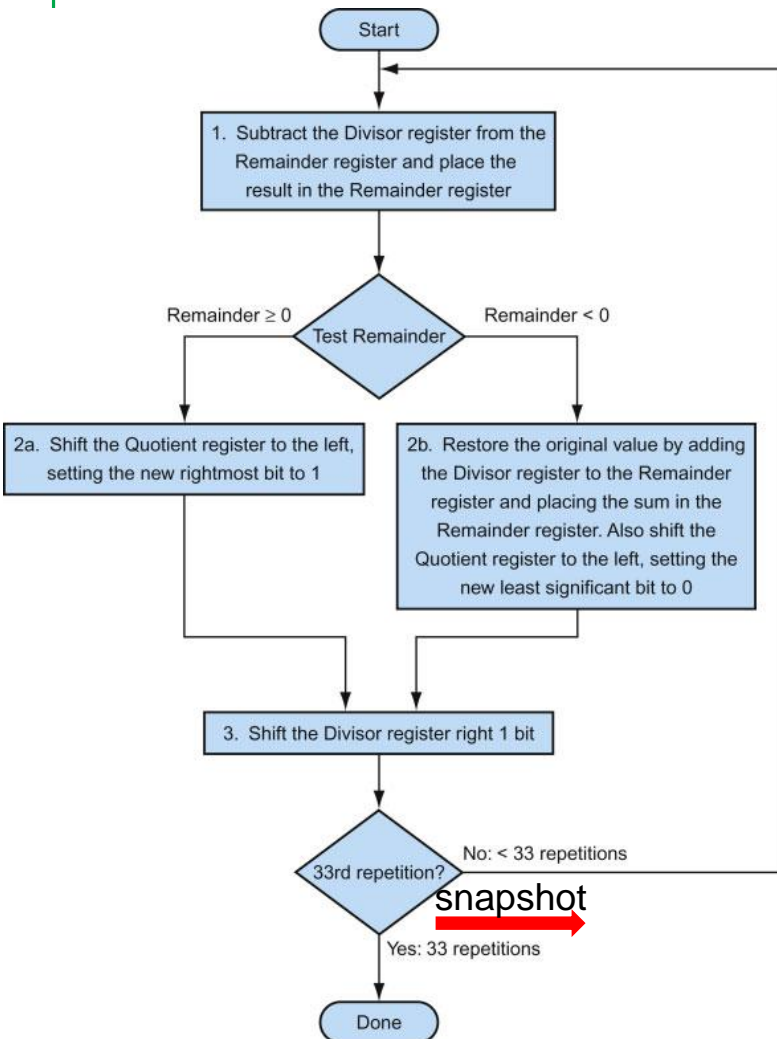
# Division Example

- Divide  $7_{\text{ten}}$  ( $0000\ 0111_{\text{two}}$ ) by  $2_{\text{ten}}$  ( $0010_{\text{two}}$ )



Done!

# Division Example


Divide  $7_{\text{ten}}$  ( $0000\ 0111_{\text{two}}$ ) by  $2_{\text{ten}}$  ( $0010_{\text{two}}$ )

Iter	Step	Quot	Divisor	Remainder
0	Initial values	0000	0010 0000	0000 0111
1	Rem = Rem – Div Rem < 0 → +Div, shift 0 into Q Shift Div right 加上他的补码	0000 0000 0000	0010 0000 0010 0000 0001 0000	1110 0111 0000 0111 0000 0111
2	Same steps as 1	0000 0000 0000	0001 0000 0001 0000 0000 1000	1111 0111 0000 0111 0000 0111
3	Same steps as 1	0000 0000 0000	0000 1000 0000 1000 0000 0100	1111 1111 0000 0111 00000111
4	Rem = Rem – Div Rem >= 0 → shift 1 into Q Shift Div right	0000 0001 0001	0000 0100 0000 0100 0000 0010	0000 0011 0000 0011 0000 0011
5	Same steps as 4	0001 0011 0011	0000 0010 0000 0010 0000 0001	0000 0001 0000 0001 0000 0001


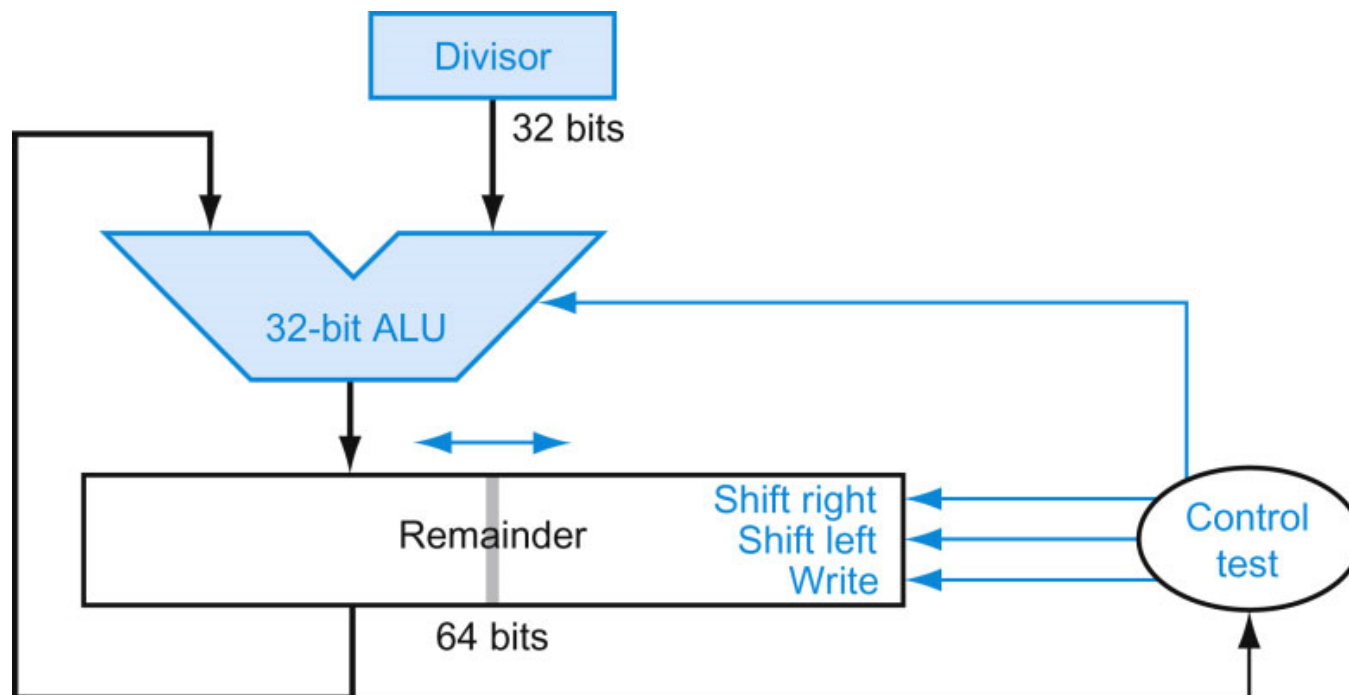
# Optimized Divider


- One cycle per partial-remainder subtraction
- Looks a lot like a multiplier!
  - Same hardware can be used for both



# Optimized Divider

Step	Remainder	Div.
0	0000	0111 0010
1.1	0000	1110
1.2	1110	1110
1.3b	0001	1100
2.2	1111	1100
2.3b	0011	1000
3.2	0001	1000
3.3a	0011	0001
4.2	0001	0001
4.3a	0010	0011
	0001	0011

开始先左移一位，然后做减法，小于0左移补0，大于0左移补1

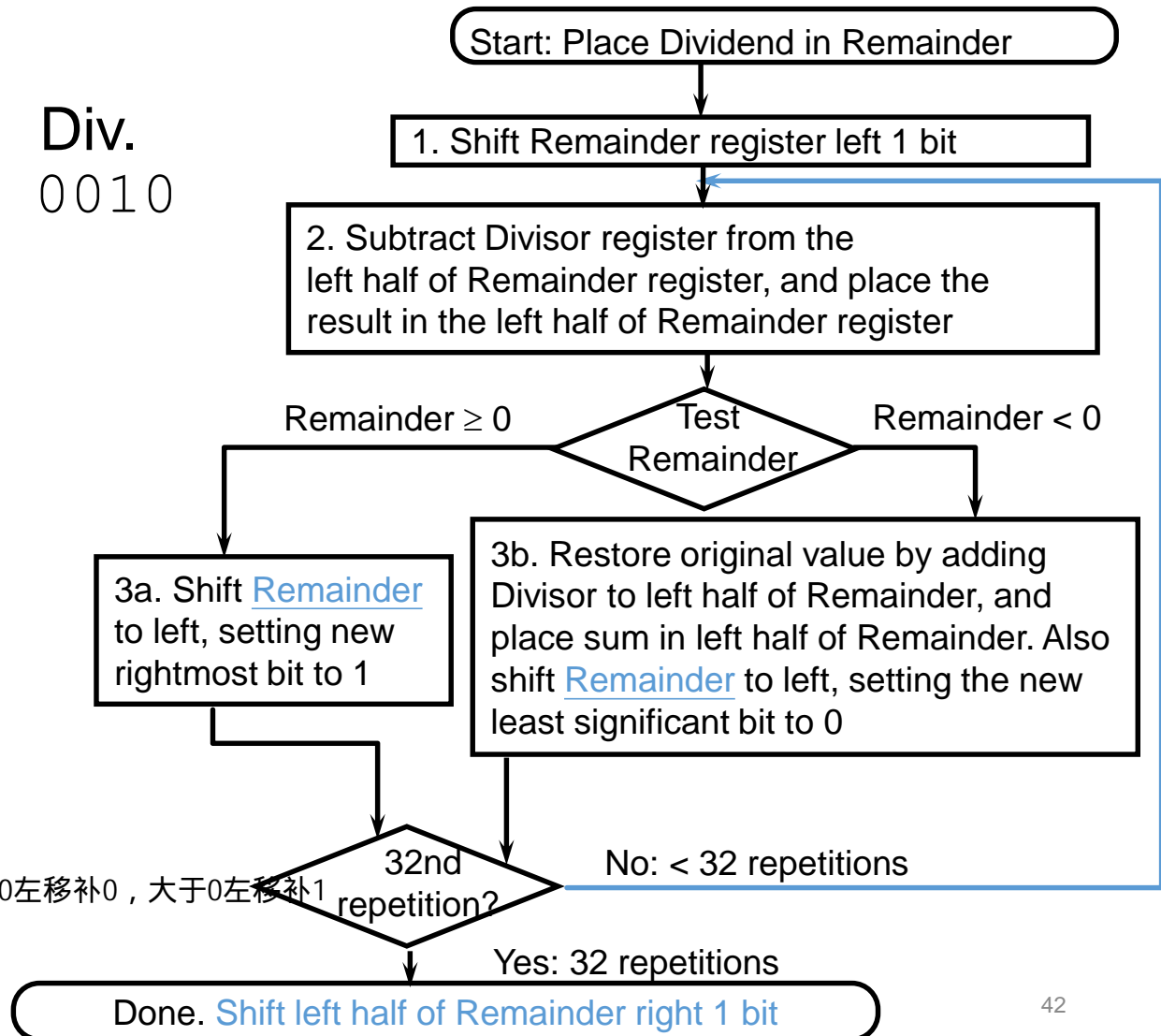

# Signed Division

- Convert to positive and adjust sign later
- Note that multiple solutions exist for the equation:  

$$\text{Dividend} = \text{Quotient} \times \text{Divisor} + \text{Remainder}$$

$$+7 \text{ div } +2 \quad \text{Quo} = +3 \quad \text{Rem} = +1$$

$$-7 \text{ div } +2 \quad \text{Quo} = -3 \quad \text{Rem} = -1$$

Why not  $-7 \text{ div } +2 \quad \text{Quo} = -4 \quad \text{Rem} = +1$ ?  
 If so,  $-(x \text{ div } y) \neq (-x) \text{ div } y \Rightarrow$  programming challenge!

$$+7 \text{ div } -2 \quad \text{Quo} = -3 \quad \text{Rem} = +1$$

$$-7 \text{ div } -2 \quad \text{Quo} = +3 \quad \text{Rem} = -1$$

- Convention:
  - Dividend and remainder have the same sign
  - Quotient is negative if signs disagree
  - These rules fulfil the equation above

# MIPS Division

- Use HI/LO registers for result
  - HI: 32-bit remainder
  - LO: 32-bit quotient
- Instructions
  - `div rs, rt` / `divu rs, rt`
  - No overflow or divide-by-0 checking
    - Software must perform checks if required
  - Use `mfhi`, `mflo` to access result