

A decorative graphic on the left side of the slide, consisting of a network of white lines and circles on a blue gradient background. The lines are vertical and horizontal, with some diagonal segments, and the circles are of varying sizes, resembling a circuit board or a digital network.

DIGITAL DESIGN

LAB10 SYNCHRONOUS SEQUENTIAL CIRCUIT-LATCH-FLIPFLOP



2022 FALL TERM @ CSE . SUSTECH

LAB10

- Synchronous sequential circuit
 - Latch
 - Flip Flops (key point of lab10)
- Verilog
 - `always@(posedge clk)` , `always@(negedge clk)` vs `always@*`
 - blocking assignment vs non-blocking assignment
- Practise

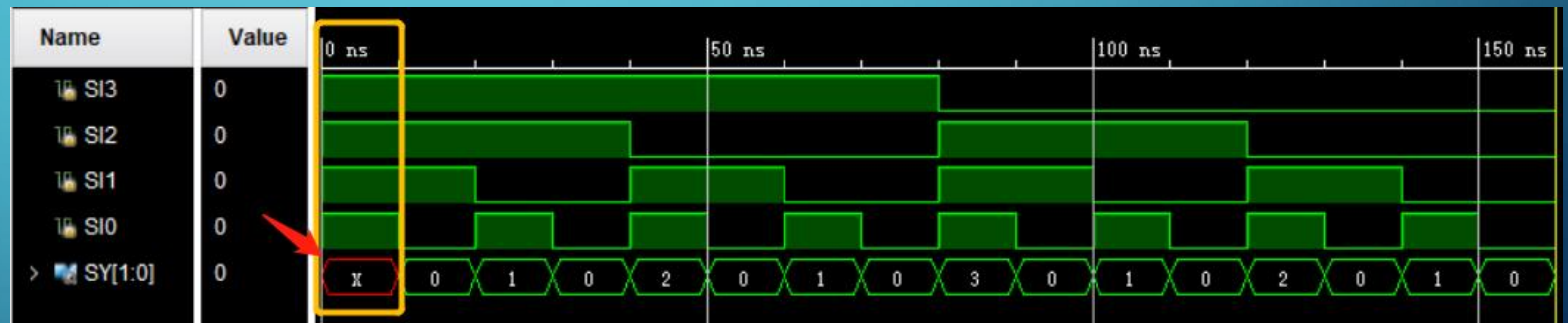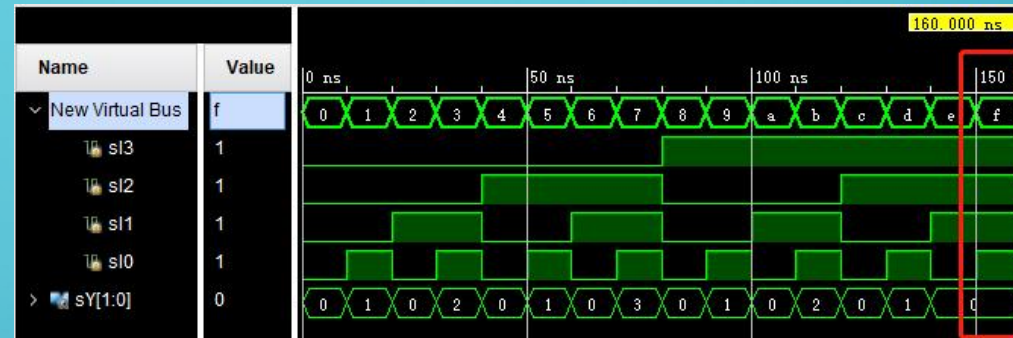4-2 PRIORITY-ENCODER IN LAB8(1)


```
//4-2 priority-encoder
module pri_encoder(
input I0, I1, I2, I3,
output reg [1:0] Y
);
always @* begin
    casex( {I3, I2, I1, I0} )
        4'bxxx0: Y=2'b00;
        4'bxxx01: Y=2'b01;
        4'bx011: Y=2'b10;
        4'b0111: Y=2'b11;
    endcase
end
endmodule
```



If there is no 'default' branch and the branch(e.g. 4'b1111 in this demo) is not list in the branches of the 'case', the circuit state will remain unchanged, and then a **latch** will be generated to save the state.

LATCH

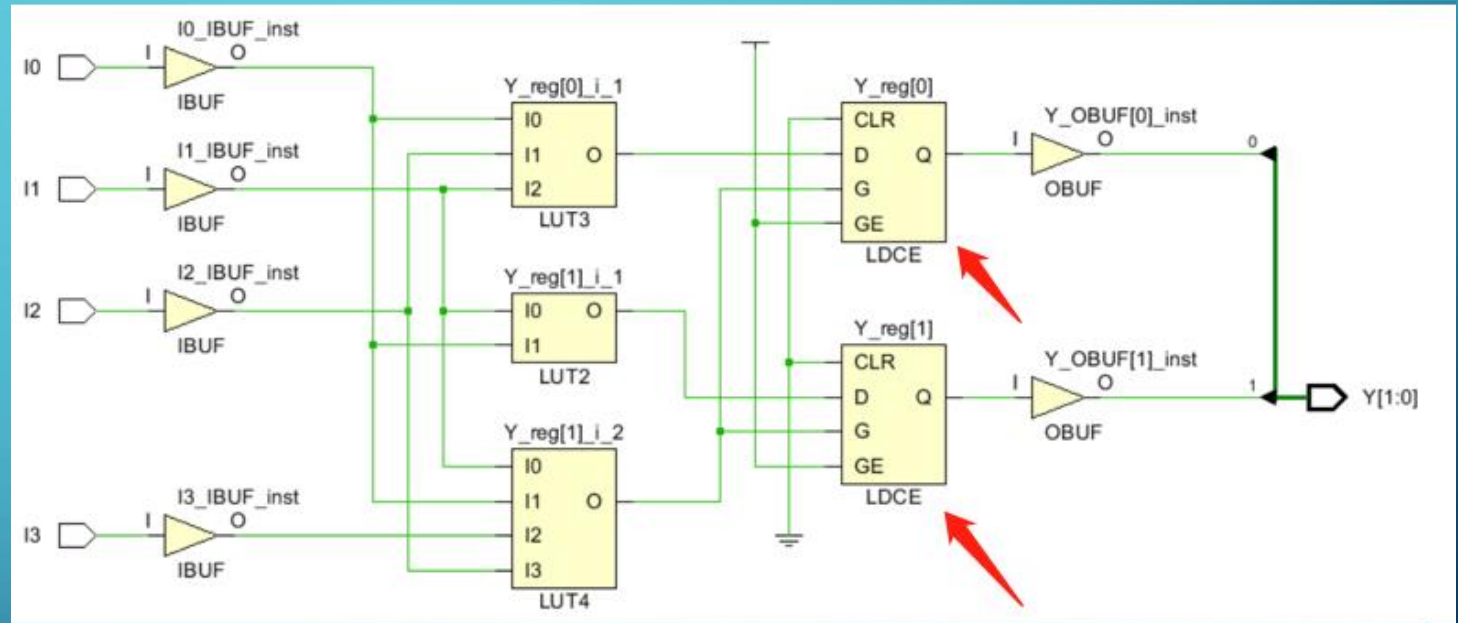
- The schematic on the right hand is the schematic of the synthesized design generated by vivado.
- **LDCE**: transparent Data **Latch** with Asynchronous Clear and Gate Enable



For more information on LDCE, please refer to *Xilinx 7 Series FPGA Libraries Guide for Schematic Design*

D LATCH

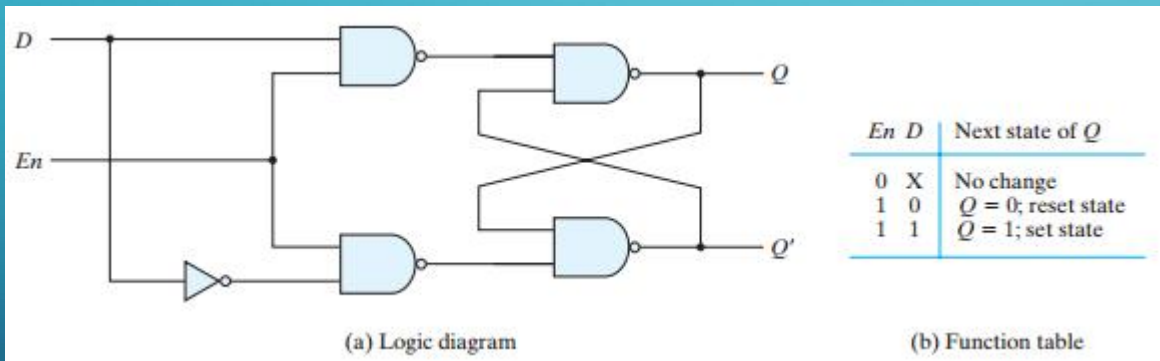- Latch: the simplest binary memory elements, static device composed of gates. When the input changes, the output changes immediately.




```
module D_Latch(  
    input En, D,  
    output reg Q,  
    output wire nQ  
);  
    assign nQ = ~Q;  
    always @*  
        if(En)  
            Q = D;  
        else  
            Q = Q;  
endmodule
```


D LATCH

- Schematic of RTL analysis:

| En | D | Next state of Q |
|----|---|-----------------------|
| 0 | X | No change |
| 1 | 0 | $Q = 0$; reset state |
| 1 | 1 | $Q = 1$; set state |

 

- Simulation result of D Latch

 

FLIP FLOP

- The storage elements (memory) used in clocked sequential circuits are called *flipflops*.
- The most economical and efficient flip-flop constructed is the edge-triggered **D flipflop**, because it requires the smallest number of gates.

 



Figure for master-slave **negative-edge** triggered D flip-flop

```
module D_ff_from_latch(  
    input clk, D,  
    output Q  
);  
    wire Y, nq_master, nq_slaver;  
    /*...*/  
    D_Latch DL_master(clk, D, Y, nq_master);  
    D_Latch DL_slaver(~clk, Y, Q, nq_slaver);  
endmodule
```



D FLIP FLOP

| Clk | Q |
|-----|-----------|
| ↑ | D |
| 0 | no change |
| 1 | no change |
| ↓ | no change |

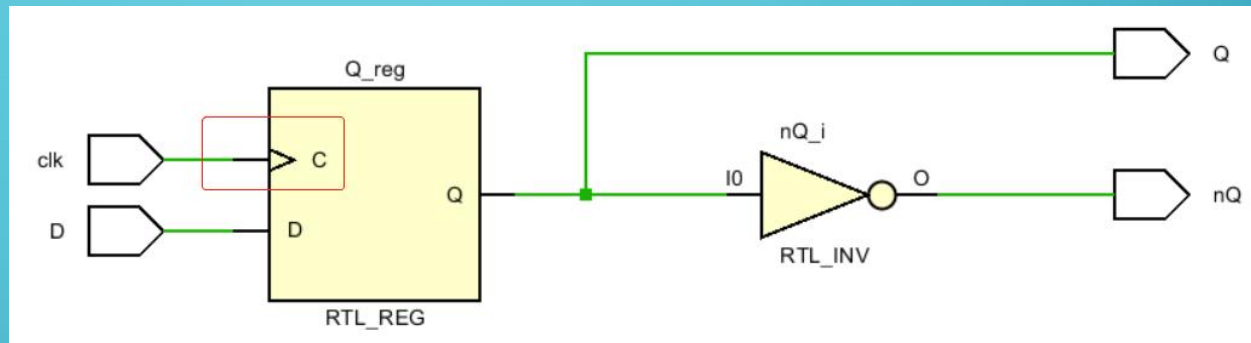

```

module D_flipflop(
input clk, D,
output reg Q,
output nQ
);
    always @(posedge clk)
        Q <= D;
    assign nQ = ~Q;
endmodule

```




JK FLIP FLOP(1)

- $Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$

| JK | | 00 | 01 | 11 | 10 |
|----------------|---|----|----|----|----|
| Q ⁿ | 0 | 0 | 0 | 1 | 1 |
| | 1 | 1 | 0 | 0 | 1 |

| J | K | Q ⁿ⁺¹ |
|---|---|------------------|
| 0 | 0 | no change |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | Q ^{n'} |

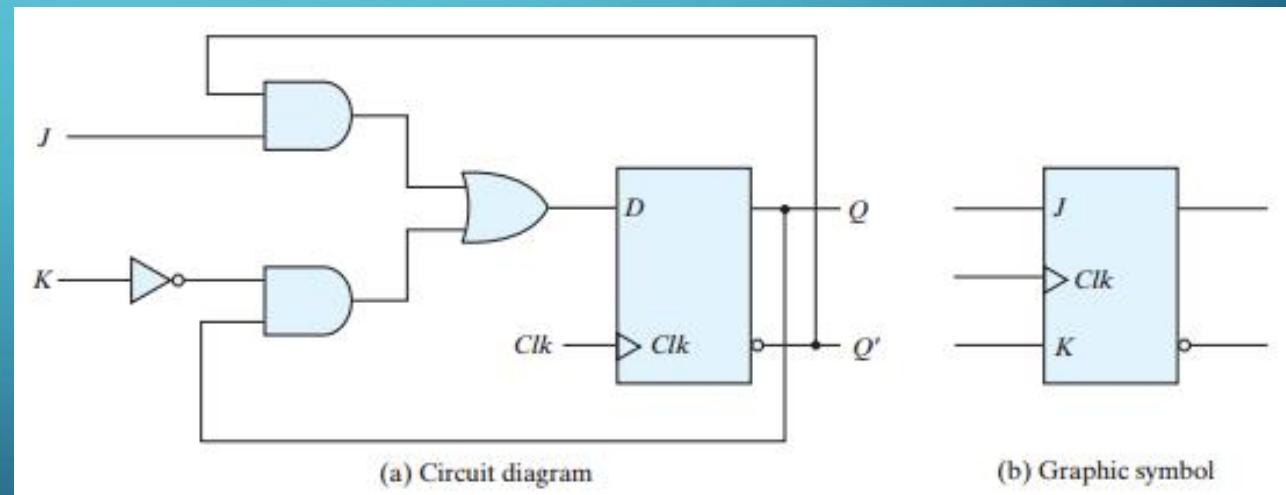

JK FLIP FLOP(2)

$$Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$$

```

module J_K_Flip_Flop(
    input Clk, J, K,
    output reg Q,
    output nQ
);
    assign nQ = ~Q;
    always @ (posedge Clk)
        case ({J, K})
            2'b10: Q<= 1'b1; //set
            2'b01: Q<= 1'b0; //reset
            2'b11: Q<= nQ;  //reverse
            2'b00: Q<= Q;   //keep
        endcase
endmodule
    
```

| J | K | Q ⁿ⁺¹ |
|---|---|------------------|
| 0 | 0 | no change |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | Q ^{n'} |



USING JK FLIP FLOP TO IMPLEMENT D FLIP FLOP


- JK Flip-Flop: $Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$
- D Flip-Flop: $Q^{n+1} = D = D\overline{Q}^n + DQ^n$

| J | K | Q^{n+1} |
|---|---|-----------|
| 0 | 0 | no change |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | Q^n |

| Clk | Q |
|-----|-----------|
| ↑ | D |
| 0 | no change |
| 1 | no change |
| ↓ | no change |


```

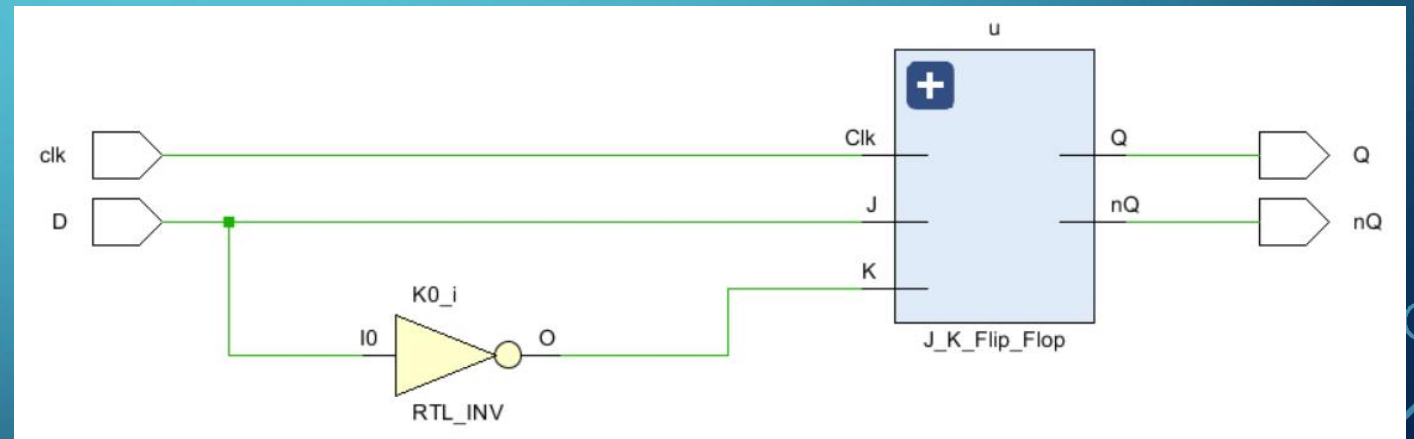module Dff_byJKff(
input clk, D,
output Q, nQ
);
    J_K_Flip_Flop u(clk, D, ~D, Q, nQ);
endmodule
    
```



T FLIP FLOP

 - The T (toggle) flip-flop is a complementing flip-flop.




| T | Q^{n+1} |
|-----|------------|
| 0 | Q^n |
| 1 | $\sim Q^n$ |

```
module T_Flip_Flop(  
    input Clk, T,  
    output reg Q,  
    output nQ  
);  
    assign nQ = ~Q;  
    always @(posedge Clk)  
        case(T)  
            1'b1: Q<= ~Q;  
            1'b0: Q<= Q;  
        endcase  
endmodule
```

USING JK FLIP FLOP TO IMPLEMENT T FLIP FLOP

 
- The T (toggle) can be obtained from a JK flip-flop when inputs J and K are tied together.



| T | Q^{n+1} |
|-----|------------|
| 0 | Q^n |
| 1 | $\sim Q^n$ |

| J | K | Q^{n+1} |
|-----|-----|-----------|
| 0 | 0 | no change |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | $Q^{n'}$ |
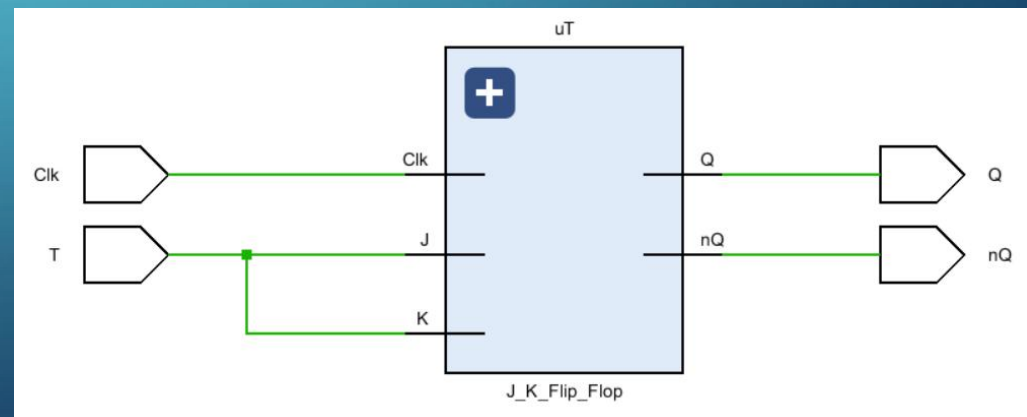
```
module Tff_by_JKff(  
    input Clk, T,  
    output Q, nQ  
);  
    J_K_Flip_Flop uT( Clk, T, T, Q, nQ);  
endmodule
```



WIRE VS REG(1)

- There are two data types in Verilog: **wire** and **register**.
 - **wire** is a kind of net, which is equivalent to physical connection.
 - **wire** is used to connects two points, and thus does **not have any driving strength**
 - **wire** data types can be used for connecting the output port to the actual driver
 - a **wire** can be assigned a value by a continuous assign statement, which is used for **designing combinational logic**
 - **default data type is wire**: this means that if you declare a port or variable without specifying reg or wire, it will be a 1-bit wide wire.
 - **reg** is a kind of register, which is equivalent to memory cell.
 - reg can **store value and drive strength**. Reg can be used for **modeling both combinational and sequential logic**.
 - **reg** data type can be driven from initial and always block.
 - The LHS of a **behavioral block(initial , always)** should be declared **as reg**
 - **input port** could drive by both wire/register, but it could ONLY be declared as wire
 - **output port** can be declared as wire or register, but it can ONLY drive wire
 - bidirectional port can only be declared as wire

NON-BLOCKING ASSIGNMENT VS BLOCKING ASSIGNMENT

- The '=' token represents a **blocking procedural assignment**
- A **combinational logic always block** should use **Blocking assignments**("=").
- The '<=' token represents a **non-blocking procedural assignment**
- A **sequential logic always block** should use **Non-blocking assignments**("<=").

NOTE: DO NOT mixing blocking assignment and non-blocking assignment in the same always block !!!

PRACTICE(1)

- Try to construct a T flipflop with a reset input.
 - There would be a reset input port apart from other inputs(clk, T), while it enable the output of T flipflop is 1'b0, while it disable the circuit works as T flipflop
 - Do the design and verify the function of your design.
 - Create the constraint file, do the synthetic and implementation, generate the bitstream file and program the device, then test on the minisys develop board.

PRACTICES(2)


$$Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$$

- Can this JK flip-flop work?
- Try to use it implement a T flip-flop, do the design, create constraint file, generate the bitstream file and program the device.
- Can the T flip-flop work? Explain the reason.

```
module J_K_Flip_Flop(  
    input Clk, J, K,  
    output reg Q, Qn  
);  
    always @(posedge Clk)  
        if({J, K} == 2'b10) //set  
            begin  
                {Q, Qn} <= 2'b10;  
            end  
        else if ({J, K}==2'b01) //reset  
            begin  
                {Q, Qn} = 2'b01;  
            end  
        else if({J, K} == 2'b11) //reverse  
            begin  
                Q <= Qn;  
                Qn <= Q;  
            end  
        end  
endmodule
```

TIPS:

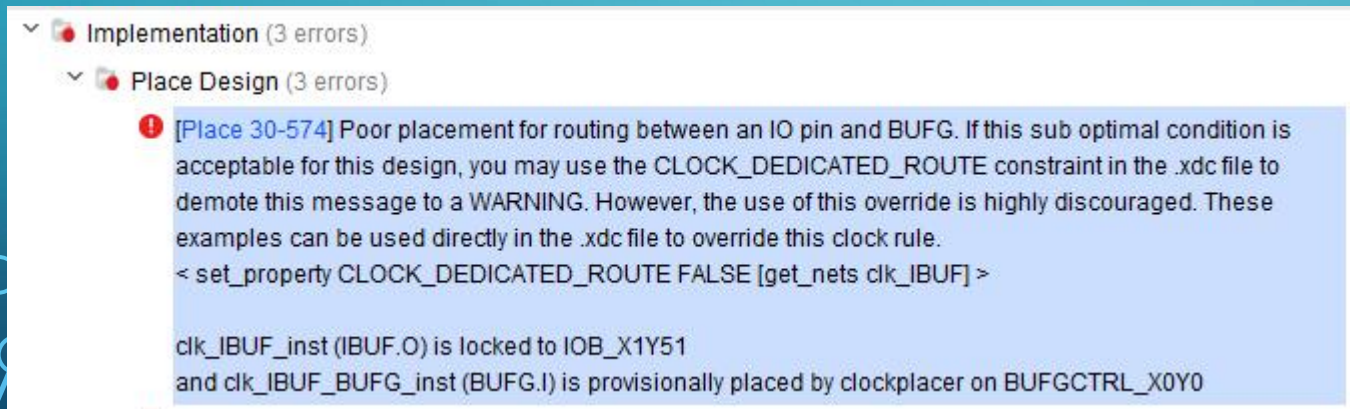- Constraints: if you want to use IO pin as clock, you should use the `CLOCK_DEDICATED_ROUTE` constraint in the .xdc file to demote the Error message to a WARNING.



```
set_property PACKAGE_PIN Y9 [get_ports clk]
set_property PACKAGE_PIN W9 [get_ports D]
set_property PACKAGE_PIN K17 [get_ports Q]
set_property PACKAGE_PIN L13 [get_ports Qn]
set_property IOSTANDARD LVCMOS33 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports D]
set_property IOSTANDARD LVCMOS33 [get_ports Q]
set_property IOSTANDARD LVCMOS33 [get_ports Qn]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets clk_IBUF]
```